

TFE4188 - Introduction to Lecture 7

Voltage regulation


Goal

Why do we need voltage regulation

Introduction to **linear regulators**

Introduction to **switched regulators**

w h y

 

Voltage source

	Chemistry	Voltage [V]
Primary Cell	LiFeS ₂ + Zn/ Alk/MnO ₂ + LiMnO ₂	0.8 - 3.6
Secondary Cell	Li-Ion	2.5 - 4.3
USB	-	4.0 - 6.5 (20)

Core

IO

Node [nm] Voltage [V]

Voltage [V]

180

1.8

5.0

130

1.5

3.0

55


1.2

1.8

22

0.8

1.2

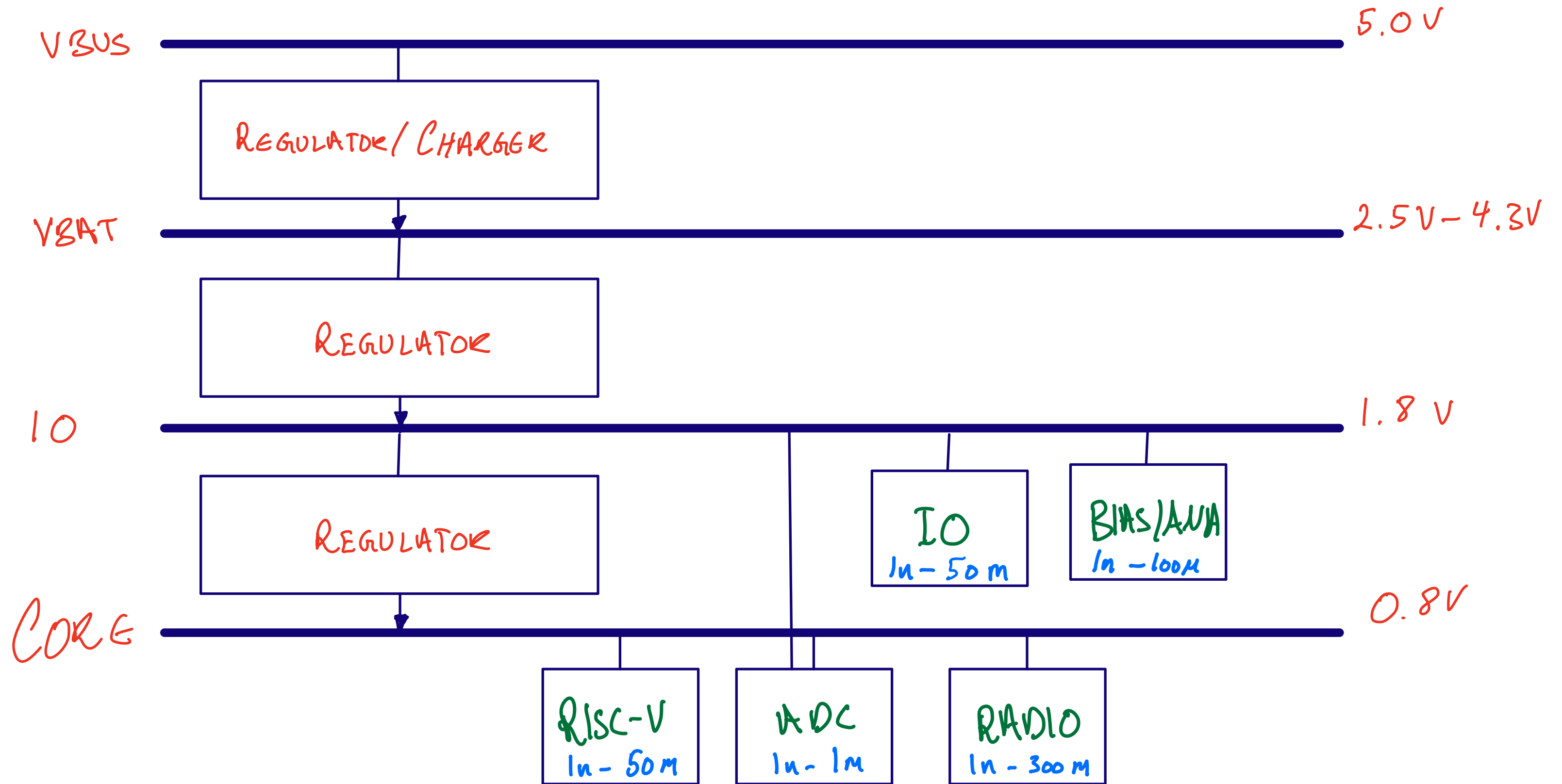

Name	Voltage	Min [nA]	Max [mA]	PWR DR [dB]
VDD_VBUS	5	10	500	77
VDD_VBAT	4	10	400	76
VDD_IO	1.8	10	50	67
VDD_CORE	0.8	10	350	75


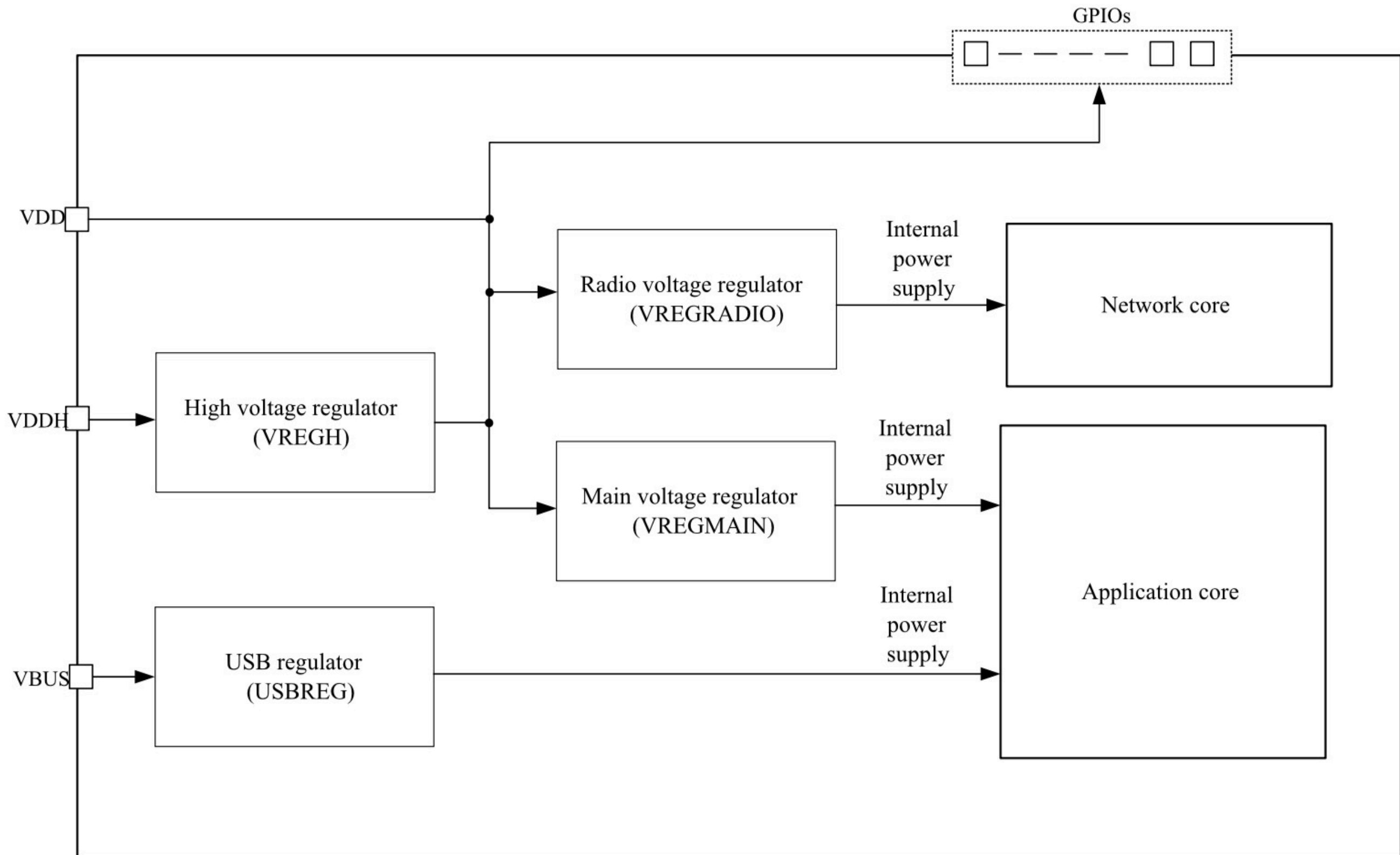



Figure 1. Regulators used in nRF5340

Linear Regulators

 

PMOS pass fet

NMOS pass fet

 

LDO's in JSSC

A Scalable High-Current High-Accuracy Dual-Loop Four-Phase Switching LDO for Microprocessors

Xiangyu Mao, Yan Lu^{id}, *Senior Member, IEEE*, and Rui P. Martins^{id}, *Fellow, IEEE*

Abstract—High-performance microprocessors need high current (ampere-level), high accuracy, and fast-response power supplies. Comparing to analog and digital low-dropout (LDO) regulators, the switching LDO can be a better candidate for such requirements, as it can drive large power transistor(s) fast and accurately. However, conventional switching LDOs need large load capacitance to reduce the output ripple, which restricts their applications. This article presents a 1.5-A fully-integrated switching LDO for microprocessors, with an easily scalable load capability. Here, we introduce three techniques together to relief

since the highest frequency core dictates the minimum V_{IN} level, other low-frequency cores will waste extra power. Fully-integrated voltage regulator can supply the local voltage domain for per-core dynamic voltage and frequency scaling (DVFS), as shown in Fig. 1 [1].

Inductor-based converters usually offer high efficiency with a high-quality factor (Q) power inductor. However, implementing high- Q inductors on silicon is challenging. In [2], buck converters have been demonstrated using on-chip induc-

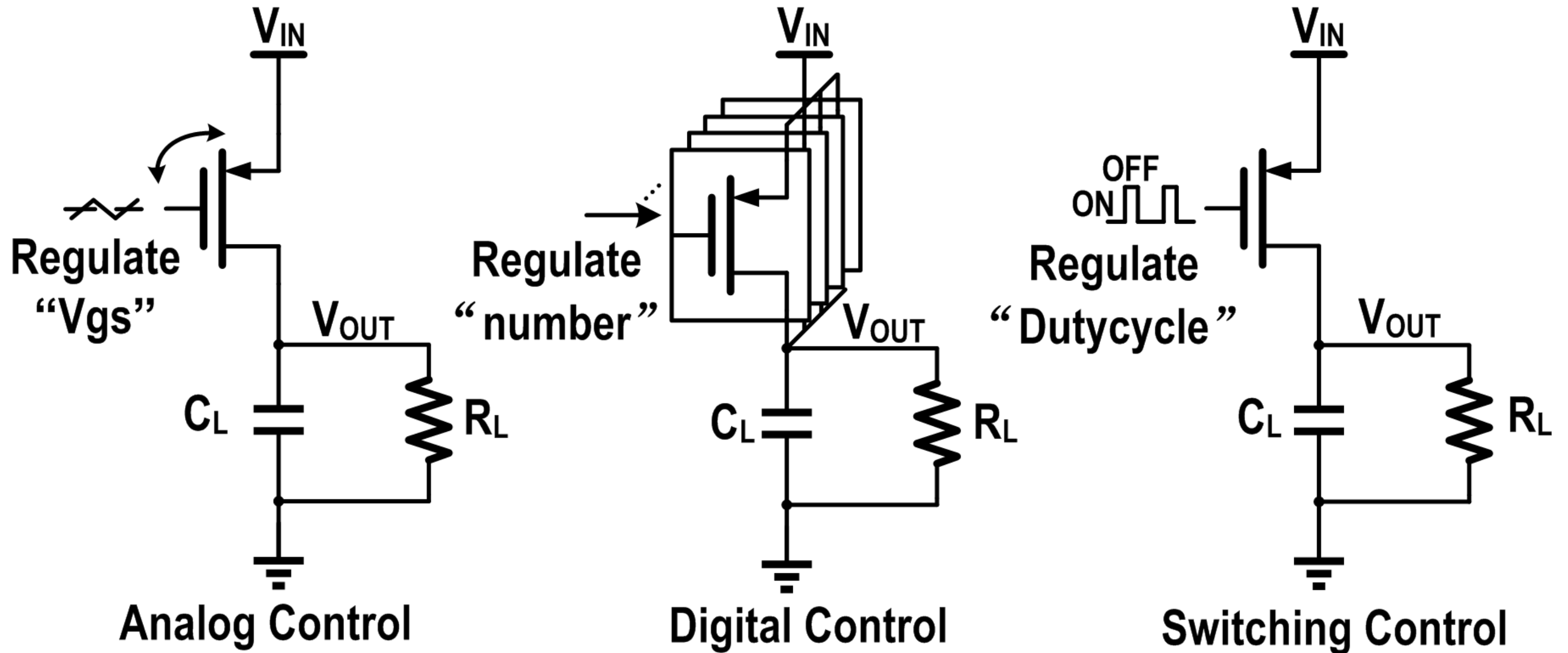


Fig. 2. LDO control methods.

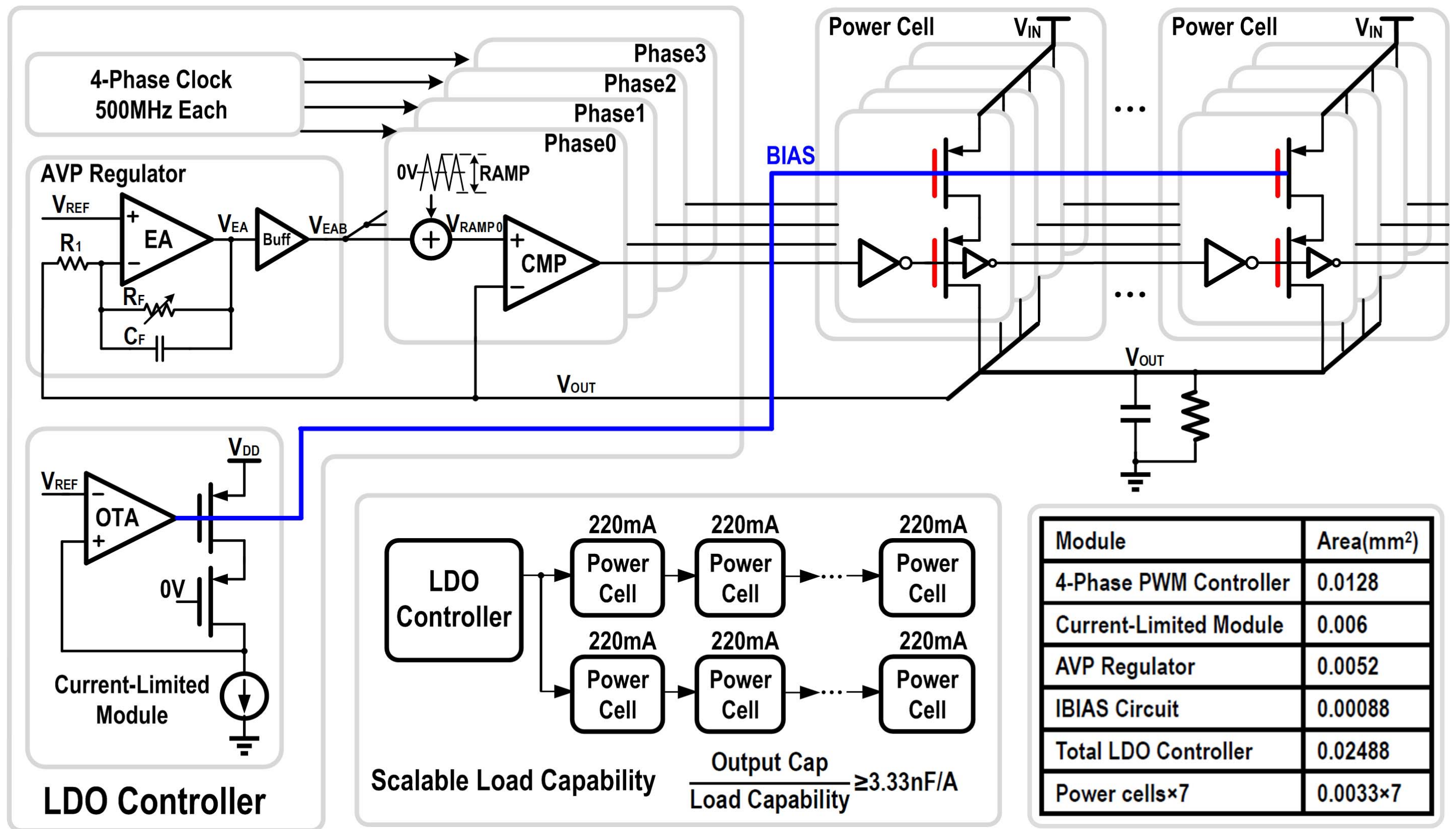


Fig. 17. System architecture of the proposed LDO with scalable load capability.

Switched Regulators

Reference Guide to Switched DC/DC Conversion

DC/DC converters convert one DC voltage level to another. Switched-mode DC/DC converters use a FET switch and a storage element to first store energy, then release it to achieve the desired output voltage. The common arrangements of switches and storage elements, or topologies, are shown below.

Non-isolated, non-inverting topologies, output voltage at same polarity as input.

Step-down or Buck converter
 $0 \leq V_{OUT} \leq V_{IN}$ $V_{OUT} = d \cdot V_{IN}$
 Simple step down circuit with single switch (FET) and storage element (inductor). The output capacitor C is needed to remove significant output ripple. Synchronous version replaces D with second FET.
 Ref: <https://www.mouser.com/applications/power-supply-topology-buck/>

Step-up or Boost converter
 $V_{OUT} \geq V_{IN}$ $V_{OUT} = V_{IN} / (1-d)$
 Simple step up circuit with single switch and storage element. The output capacitor C is needed to remove significant output ripple. Synchronous version replaces D with second FET.

SEPIC (Single-ended primary-inductor converter)
 $V_{OUT} = d \cdot V_{IN} / (1-d)$
 Can step-up or step down as required to maintain a fixed output voltage. Vout is fixed by the switching duty cycle. Can use coupled inductors to save PCB space.

Non-isolated, inverting topologies – output voltage polarity reversed vs input

Inverting (buck-boost)
 $V_{OUT} = -d \cdot V_{IN} / (1-d)$
 Simple single switch and inductor topology. Maintains a stable but inverted output voltage, with varying input voltage. The output capacitor C is needed to remove significant output ripple.

Ćuk (Pronounced 'Chook')
 $V_{OUT} = -d \cdot V_{IN} / (1-d)$
 A buck-boost topology with inverted output voltage and very low ripple current. Can use coupled inductors to save PCB space. Ideal for applications needing stable smooth output from varying input source.
 Note: The output current is continuous and ripple-free

Isolated Topologies

Forward converter
 $V_{OUT} = V_{IN} \cdot d \cdot (N_s/N_p)$
 Can provide Vout higher or lower than Vin and electrical isolation via a transformer. Higher output power (generally up to 200W) along with higher energy efficiency than Flyback topology.
 Ref: <https://www.mouser.com/applications/power-supply-topology-forward/>

Push-pull (Half Bridge)
 $V_{OUT} = 2 \cdot V_{IN} \cdot d \cdot (N_s/N_p)$
 Can provide Vout higher or lower than Vin, gives electrical isolation via a transformer, output power up to 500W along with higher energy efficiency than Flyback topology.
 Ref: <https://www.mouser.com/applications/power-supply-topology-half/>

Full bridge
 $V_{OUT} = 2 \cdot V_{IN} \cdot d \cdot (N_s/N_p)$
 A robust buck converter topology, similar to half-bridge, can provide Vout higher or lower than Vin. Often used in higher power applications such as EV charging and renewable energy systems.

Flyback
 $V_{OUT} = V_{IN} / (1-d)$
 Simple single transistor topology, typically used for offline, low output power (<100W) applications such as cellphone chargers. Fixed Vout determined by transformer.
 Ref: <https://www.mouser.com/applications/power-supply-topology-flyback/>

Charge Pumps DC/DC converters that use capacitors as the storage element are known as Charge Pumps. Suitable for low-power applications, they are typically used to boost or invert input voltage. They may be cascaded in order to obtain even-numbered multiples or fractions.


Voltage doubling charge pump
 $V_{OUT} = 2 \cdot V_{IN} - 2 \cdot V_D$
 (Where V_D is the voltage drop across the diodes)

Inverting charge pump
 $V_{OUT} = -V_{IN} + 2 \cdot V_D$
 (Where V_D is the voltage drop across the diodes)

Disclaimer: These diagrams are for reference only and not intended to be implemented as complete working designs. The simplified equations shown are for ideal converters and do not account for losses that may occur within components.

Reference Guide to Switched DC/DC Conversion

Inductive DC/DC converters


 



$$I_x(t) = \frac{1}{L} \int V_x(t) dt$$

$$V_o(t) = \frac{1}{C} \int (I_x(t) - I_o(t)) dt$$


Pulse width modulation (PWM)

Jupyter PWM BUCK model

  


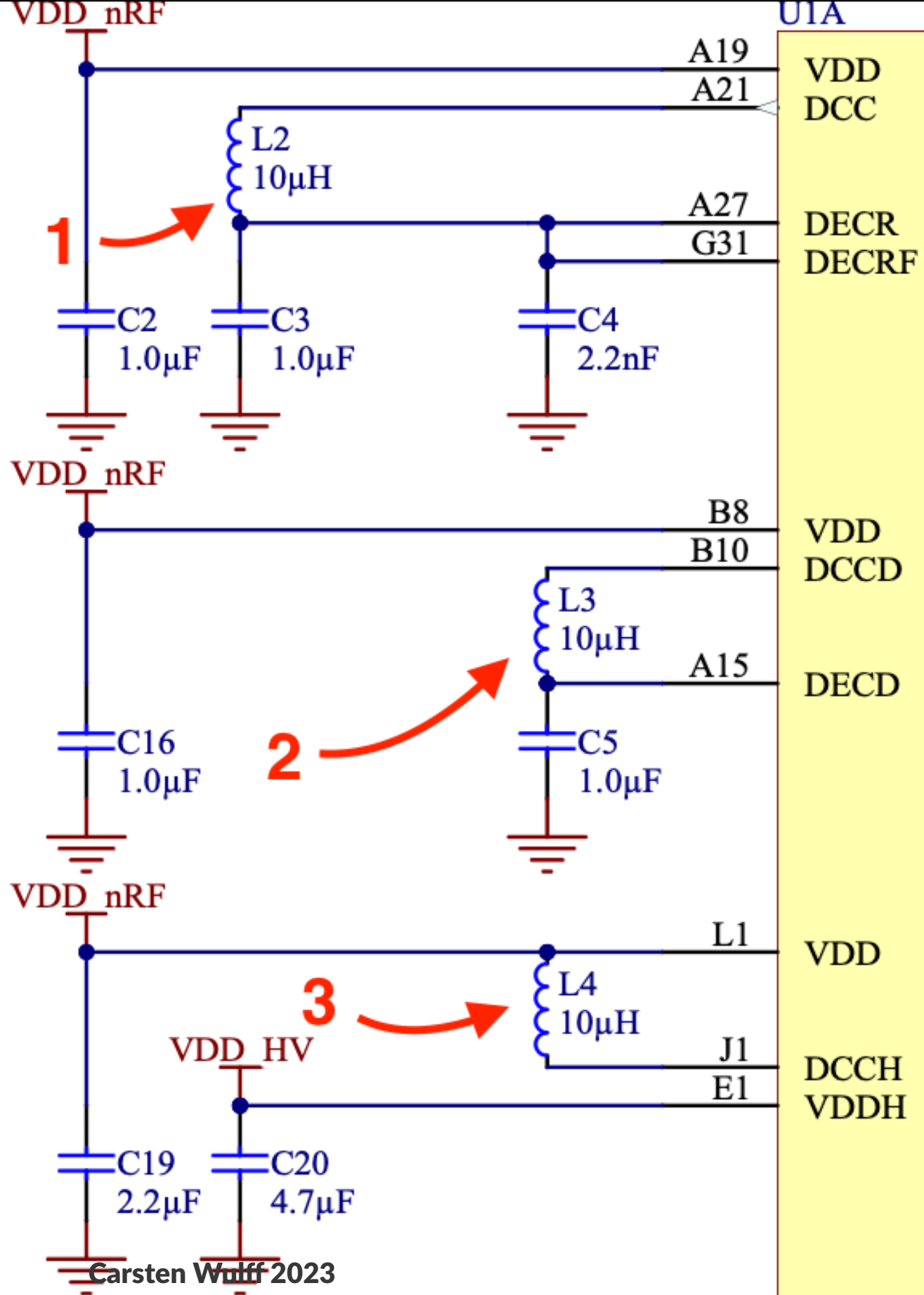


nRF5340


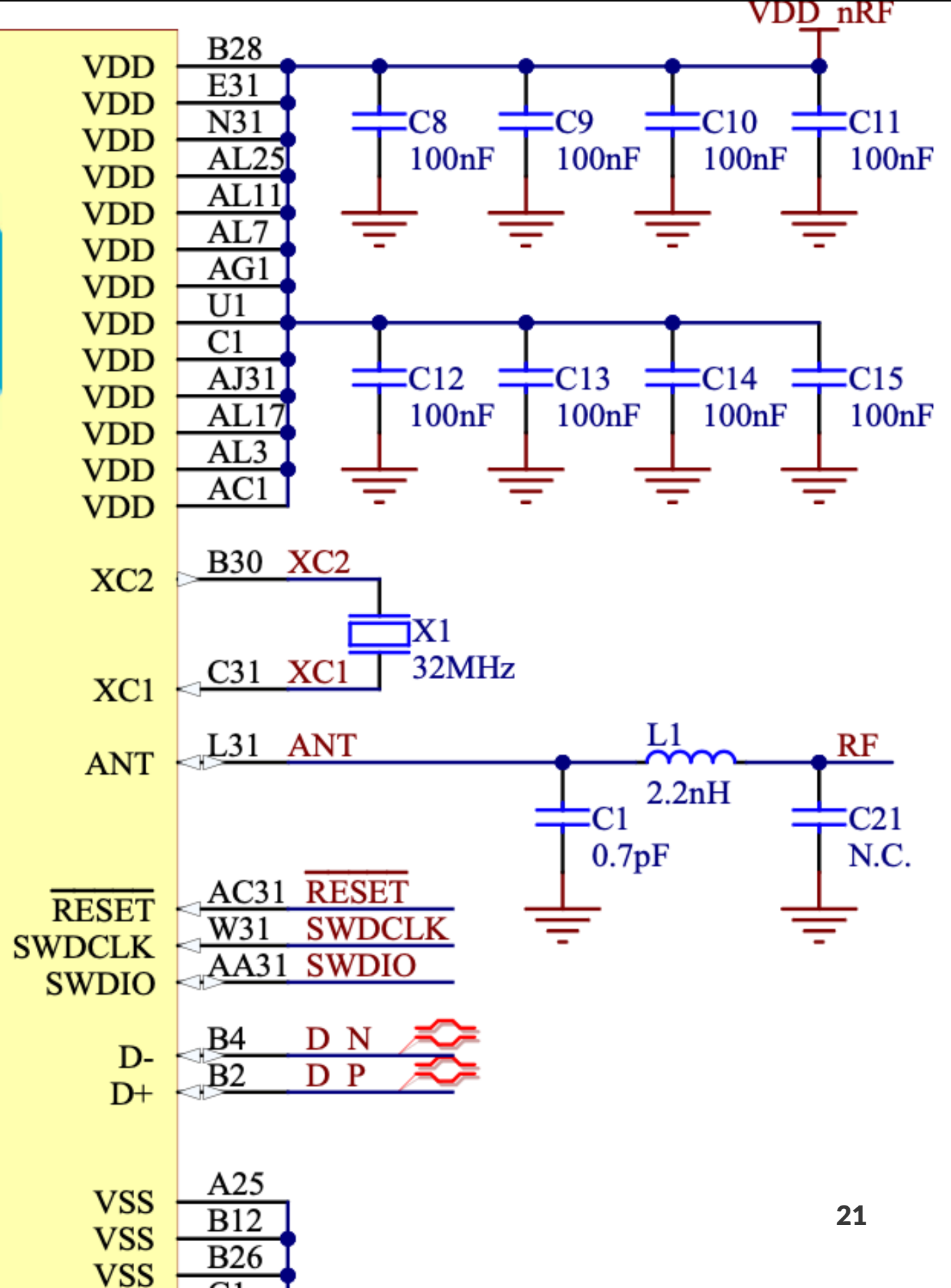


Pulsed Frequency Mode (PFM)

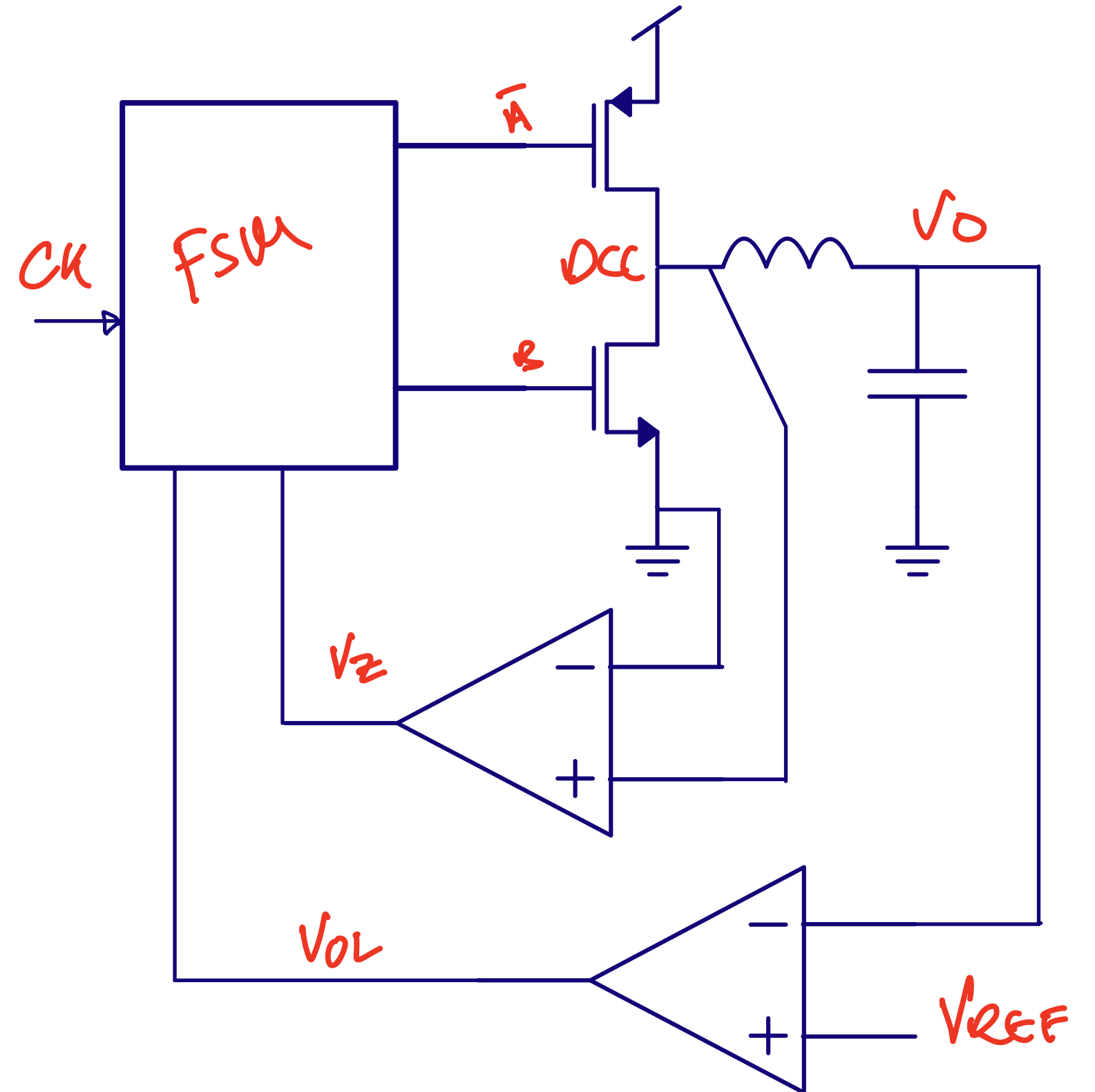

 

Jupyter PFM BUCK model

 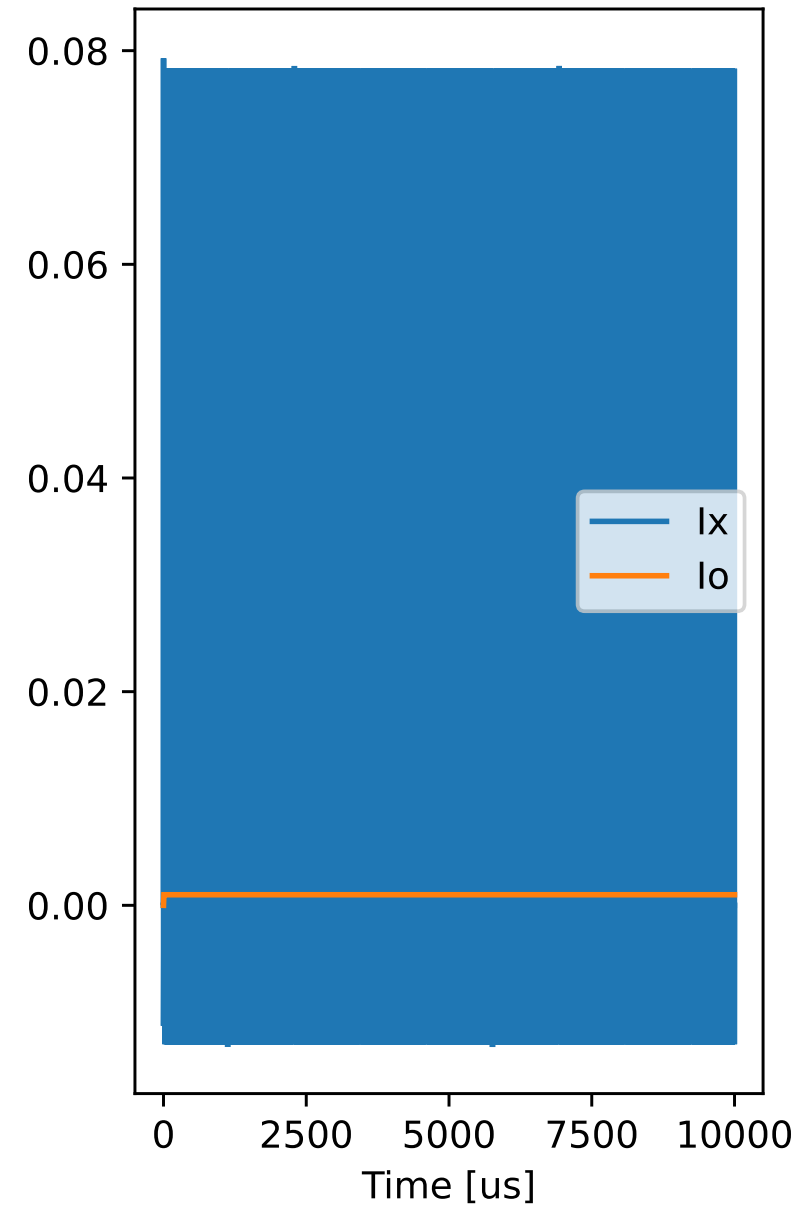

BUCKs in JSSC

A 10-MHz 2–800-mA 0.5–1.5-V 90% Peak Efficiency Time-Based Buck Converter With Seamless Transition Between PWM/PFM Modes

814

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 53, NO. 3, MARCH 2018

A 10-MHz 2–800-mA 0.5–1.5-V 90% Peak Efficiency Time-Based Buck Converter With Seamless Transition Between PWM/PFM Modes

Seong Joong Kim¹, Woo-Seok Choi¹, Robert Pilawa-Podgurski, and Pavan Kumar Hanumolu, *Member, IEEE*

Abstract—Time-based controllers are well suited for implementing both single- and multi-phase wide bandwidth high switching frequency pulsewidth modulation (PWM)-based dc–dc converters. They also consume very little quiescent current but their light load efficiency is severely degraded by switching losses. We explore pulse frequency modulation (PFM) that is commonly used to improve light load efficiency in voltage-mode controllers and extend its operation to time-based controllers. To maintain high efficiency even in the presence of dynamic load variations, we present techniques to perform automatic and seamless switching between PWM/PFM modes. Fabricated in a 65-nm CMOS, the prototype buck converter using the time-based PWM/PFM control achieves 90% peak efficiency and >80% efficiency over a load current range of 2–800 mA. Output voltage changes by less than 40 mV during PWM to PFM transitions.

Index Terms—Buck converter, high switching frequency, light load efficiency, mode switching, pulse frequency modulation (PFM), pulsewidth modulation (PWM), time-based control.

I. INTRODUCTION

the need for a wide bandwidth error amplifier, a pulsewidth modulation (PWM) in analog controllers or a high-resolution analog-to-digital converter (ADC), and a digital PWM in digital controllers. Time-based controller was also shown to be very effective for implementing high-efficiency multi-phase converters [9]. By generating multi-phase control signals with precisely matched duty cycles, a time-based approach achieves implicit passive current matching [9] needed for maximizing efficiency [10], [11]. To summarize, the time-based control enables high F_{sw} compact dc–dc converters that consume low quiescent current and achieve high efficiency over a wide range of load currents through multi-phase operation. However, large switching losses that come with high F_{sw} severely degrade efficiency under light load conditions. Consequently, efficiency of state-of-the-art time-based buck converters deteriorates significantly at light loads (<50 mA) [8], [9]. Because efficiency under light load condition has significant impact on battery

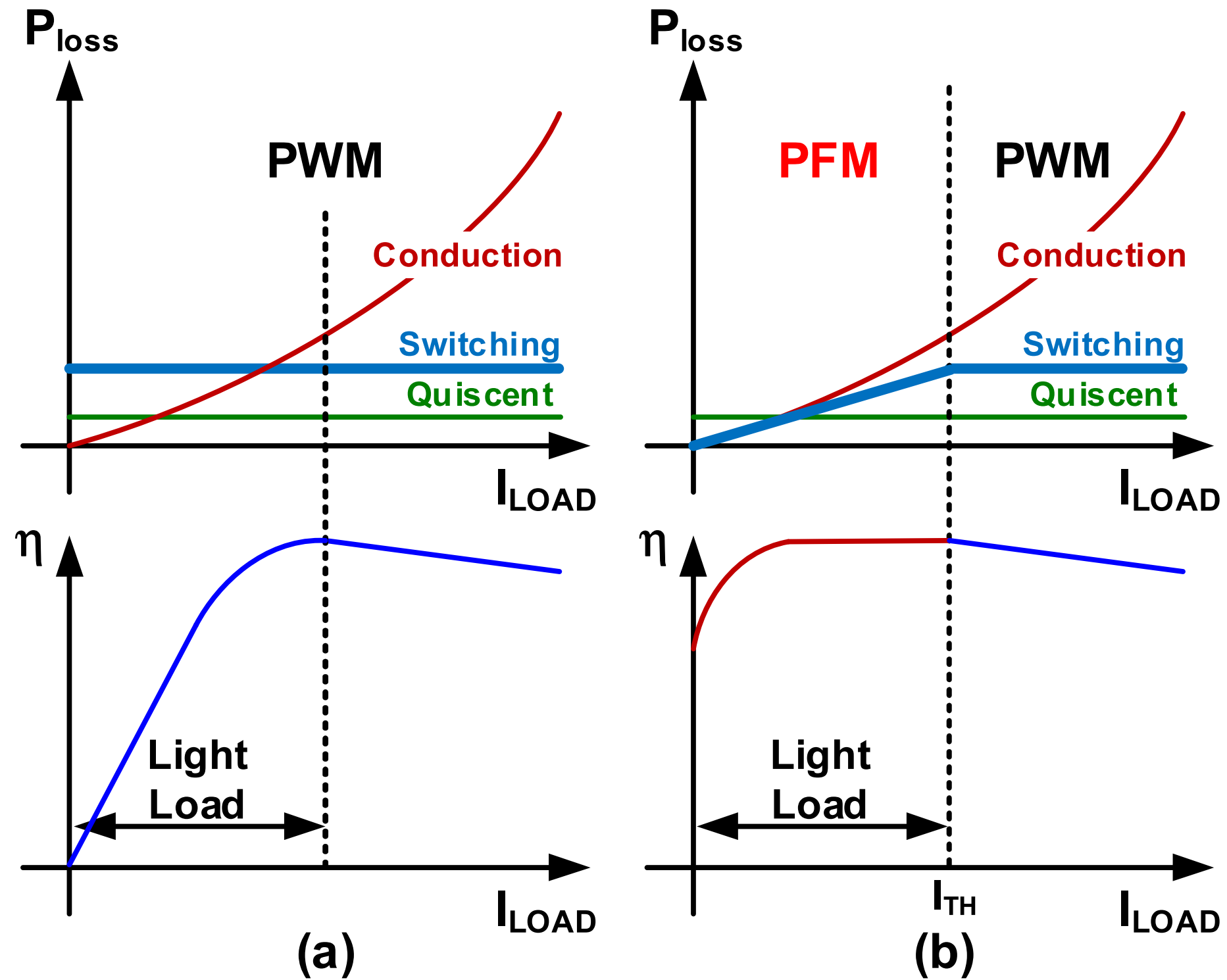


Fig. 1. Loss components and efficiency verses load current in (a) PWM mode and (b) PFM mode.


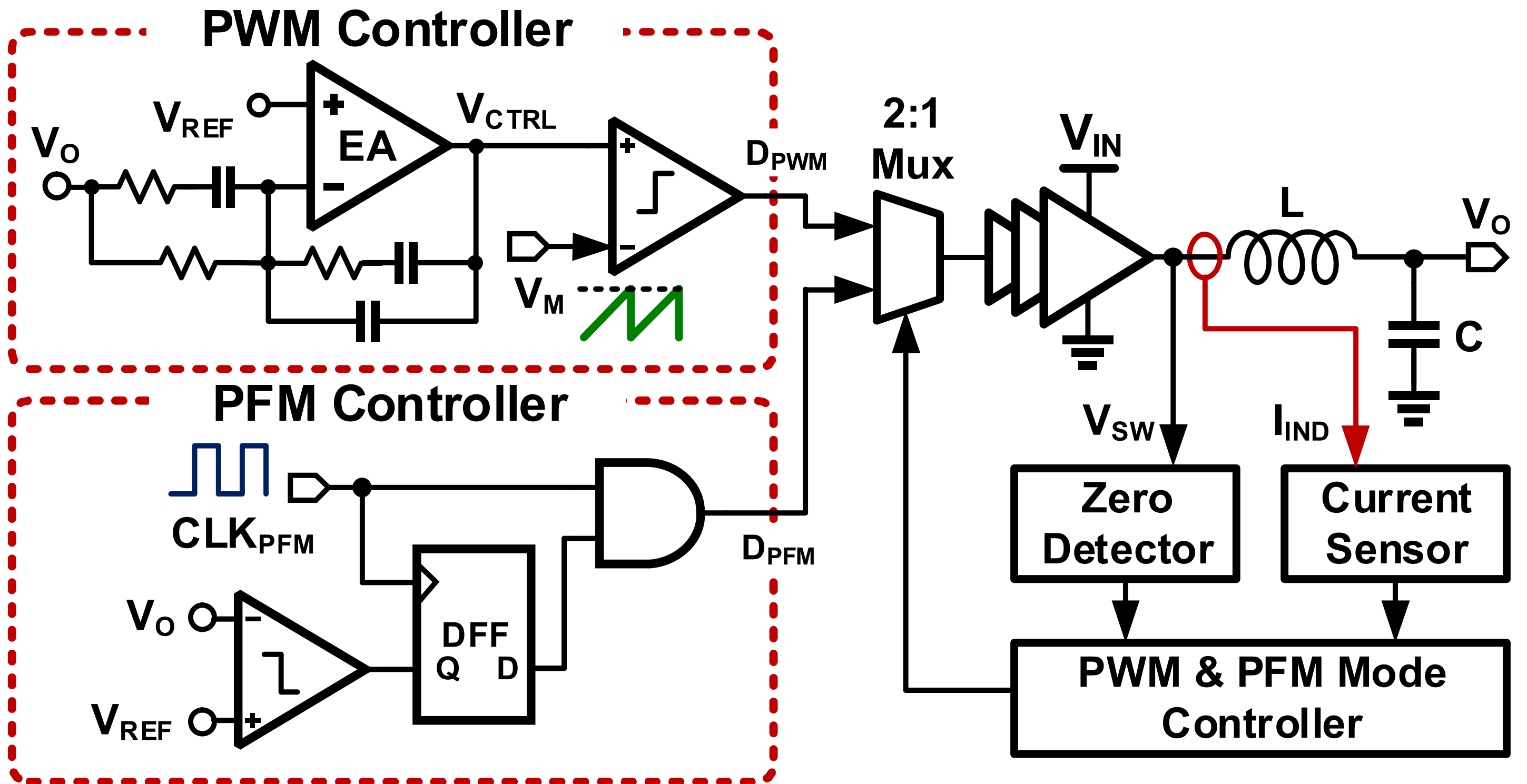


Fig. 7. Simplified buck converter that uses both PWM and PFM modes.
 Carsten Wulff 2023 28

Boost

 

$$V_D = \frac{V_{in}}{1 - \text{Duty}}$$

Thanks!