

date: 2024-03-14

TFE4188 - Lecture 9

# Oscillators

# Goal

Why

Introduction to **Crystal Oscillators**

Introduction to **VCOs**

Introduction to **Relaxation-oscillators**

**Why**

I just want the most precise clock  
that can be made !!!

# Atomic clocks

## Cesium standard

The second is defined by taking the fixed numerical value of the cesium frequency  $\nu_{\text{Cs}}$ , the unperturbed ground-state hyper-fine transition frequency of the cesium 133 atom, to be 9 192 631 770 when expressed in the unit Hz, which is equal to  $\text{s}^{-1}$


# Microchip 5071B Cesium Primary Time and Frequency Standard



- $< 5E-13$  accuracy high-performance models
- Accuracy levels achieved within 30 minutes of startup
- $< 8.5E-13$  at 100s high-performance models
- $< 1E-14$  flicker floor high-performance models

"Ask for a quote" => The price is really high, and we don't want to tell you yet


# Rubidium standard

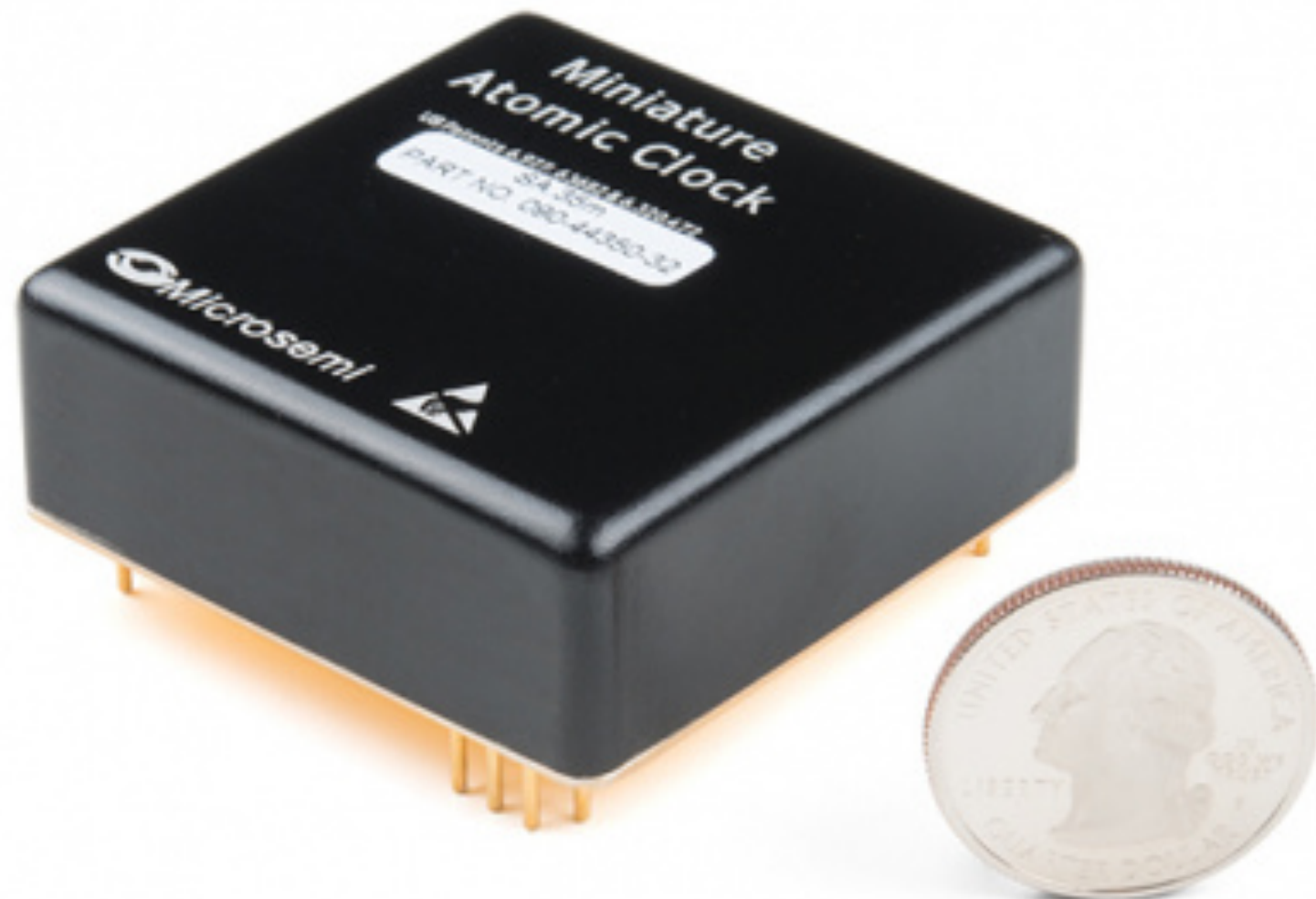

[Rubidium standard](#), use the rubidium hyper-fine transition of 6.8 GHz (6834682610.904 Hz)


*The MAC is a passive atomic clock, incorporating the interrogation technique of Coherent Population Trapping (CPT) and operating upon the D1 optical resonance of atomic Rubidium Isotope 87.*

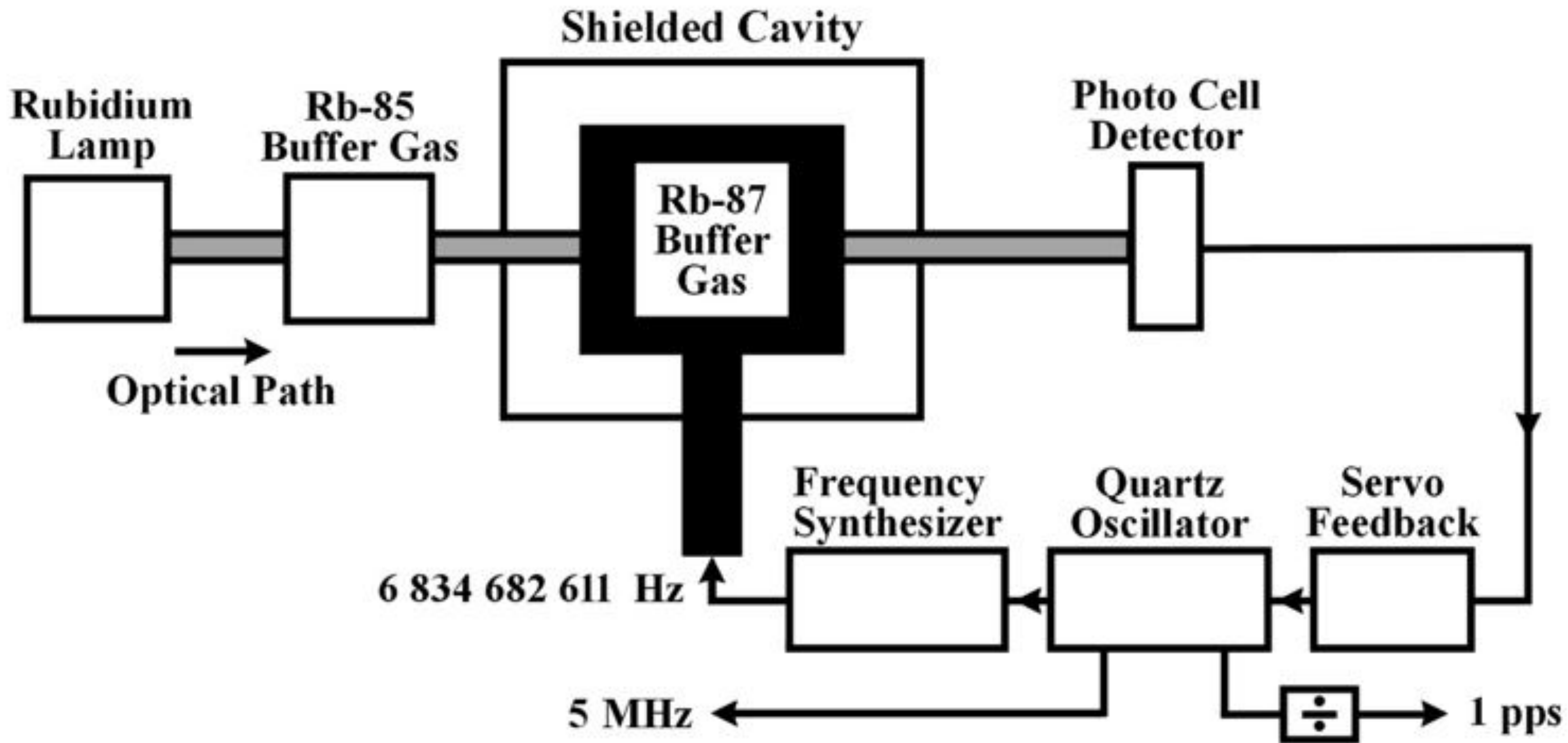
**A rubidium clock is basically a crystal oscillator locked to an atomic reference.**






# Crystal oscillators

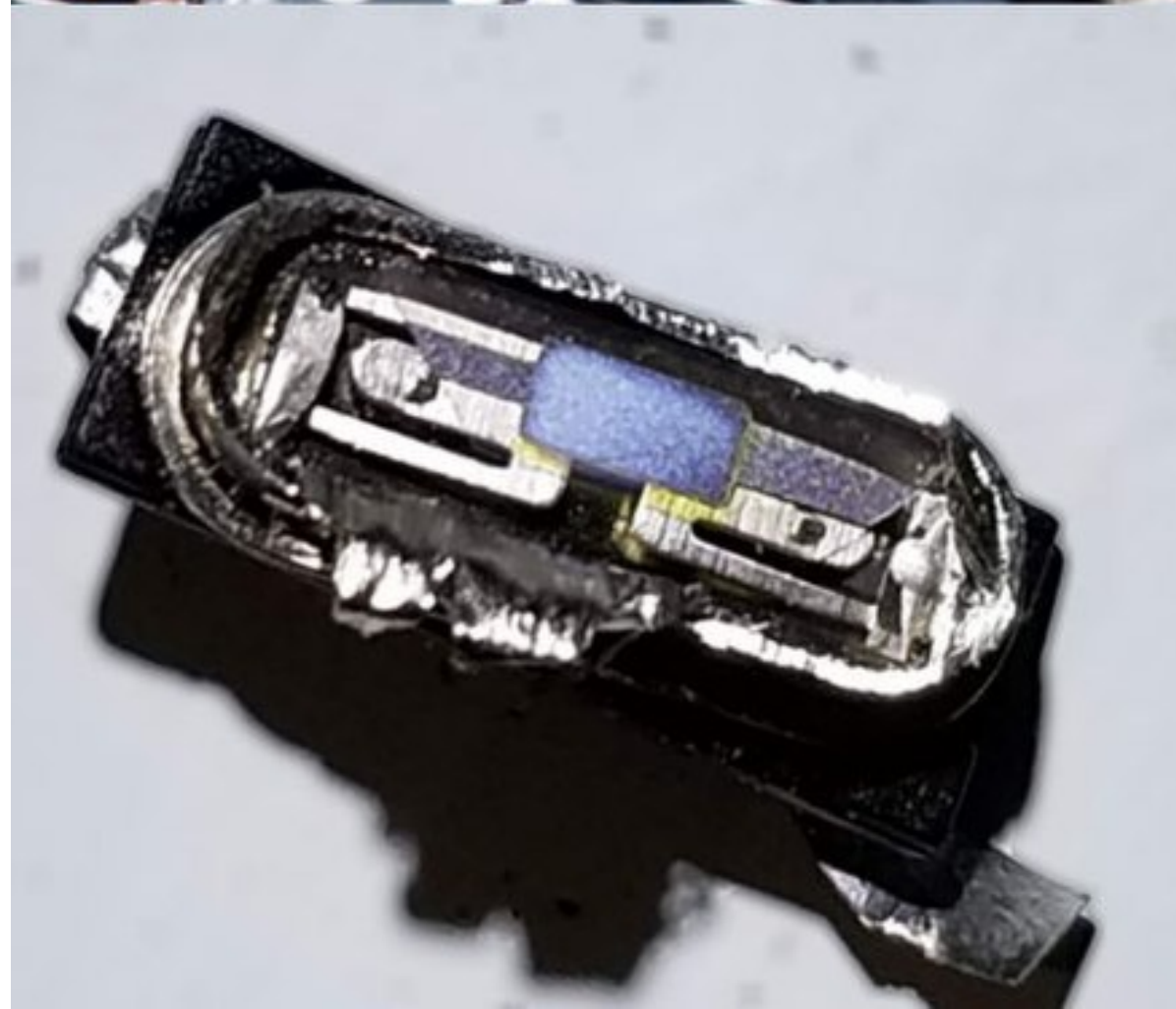


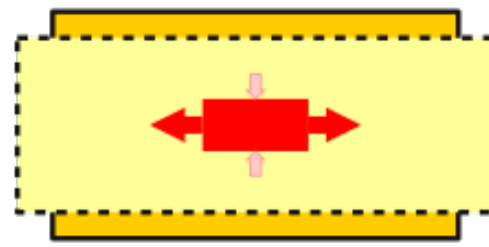


Longitudinal mode

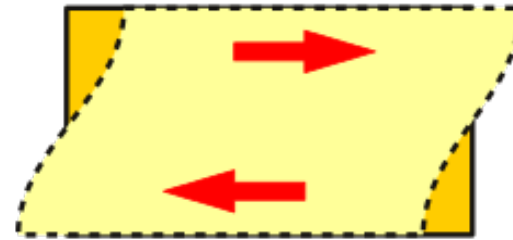

Thickness shear mode

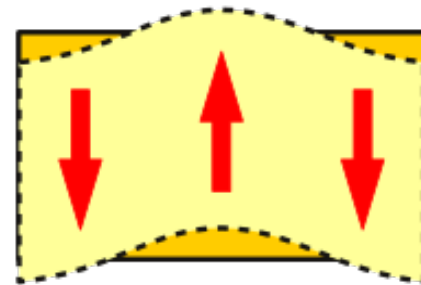

Flexural mode

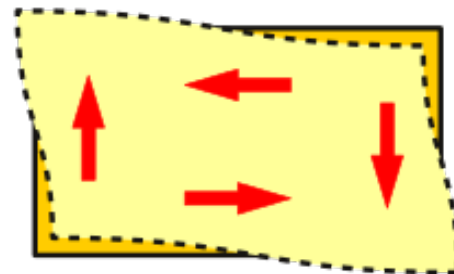


Face shear mode



Tuning fork

$$R = R_s + sL + \frac{1}{sC_F}$$

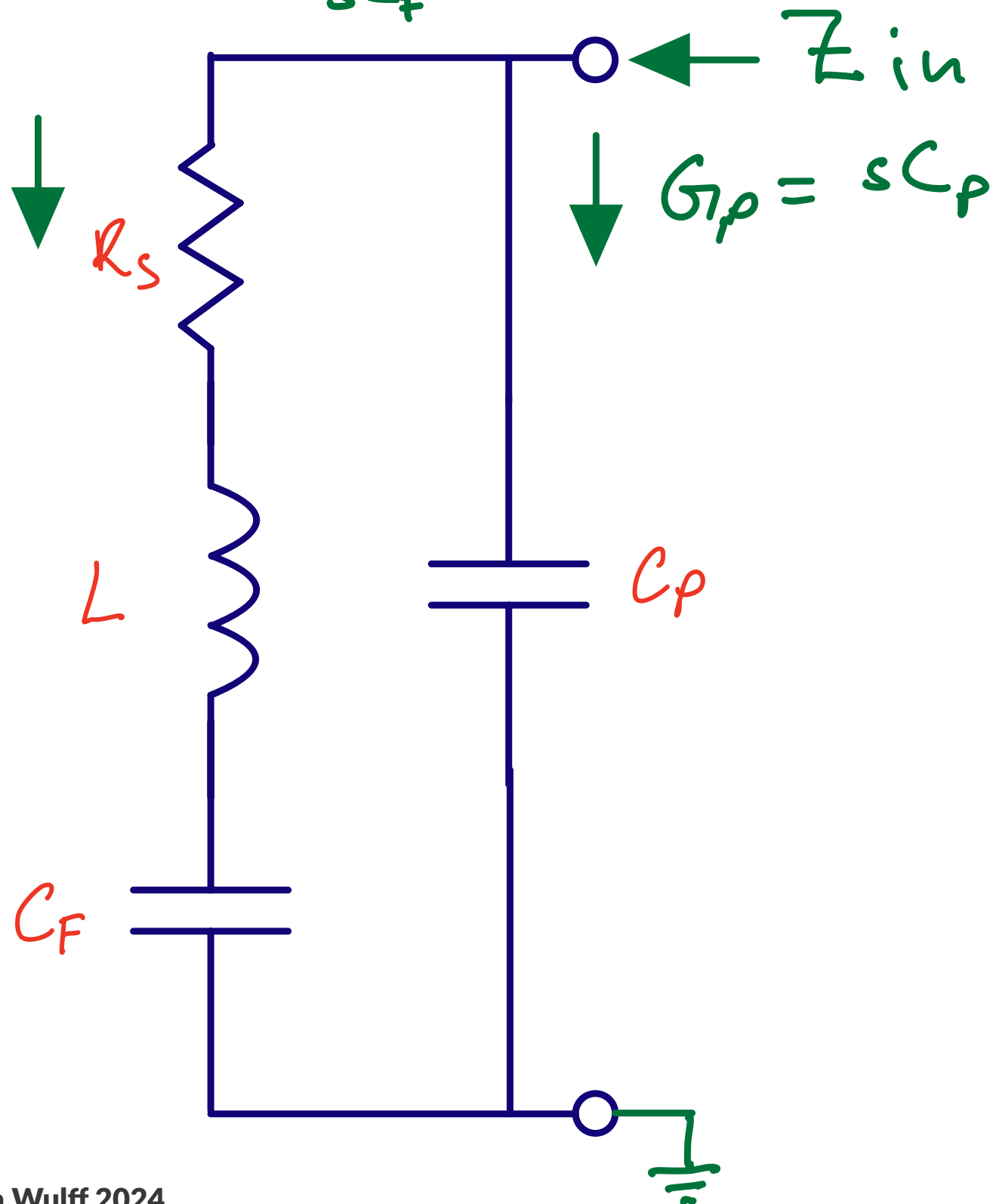



Assuming zero series resistance

$$Z_{in} = \frac{s^2 C_F L + 1}{s^3 C_P L C_F + s C_P + s C_F}$$

Since the  $1/(sC_p)$  does not change much at resonance, then

$$Z_{in} \approx \frac{L C_F s^2 + 1}{L C_F C_p s^2 + C_F + C_P}$$

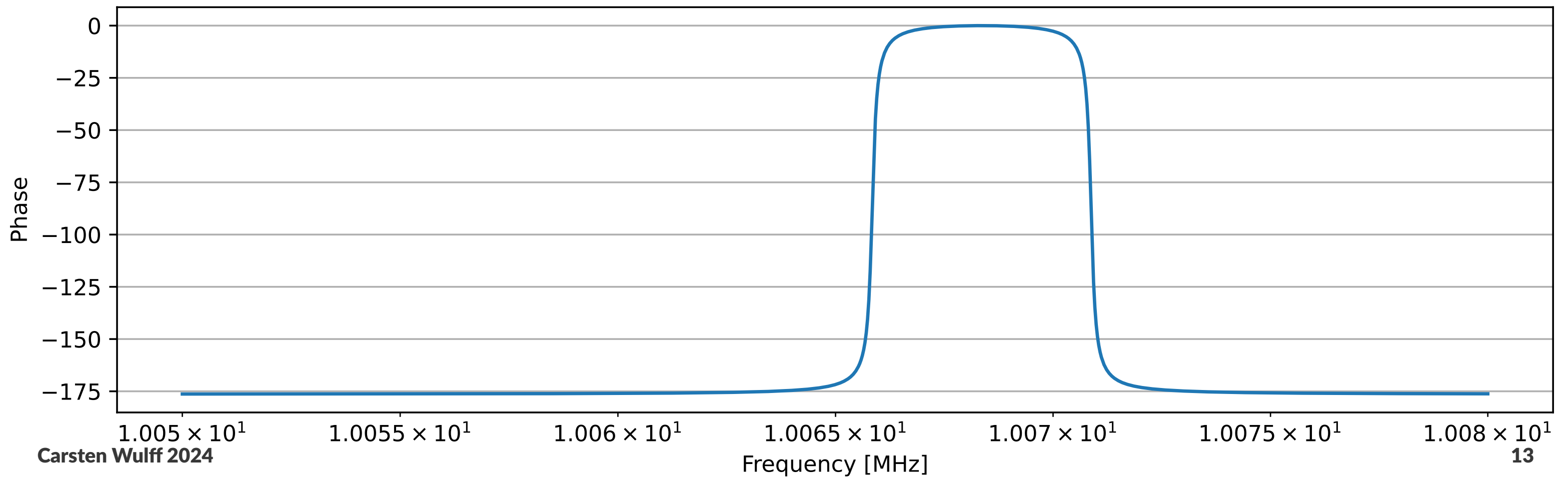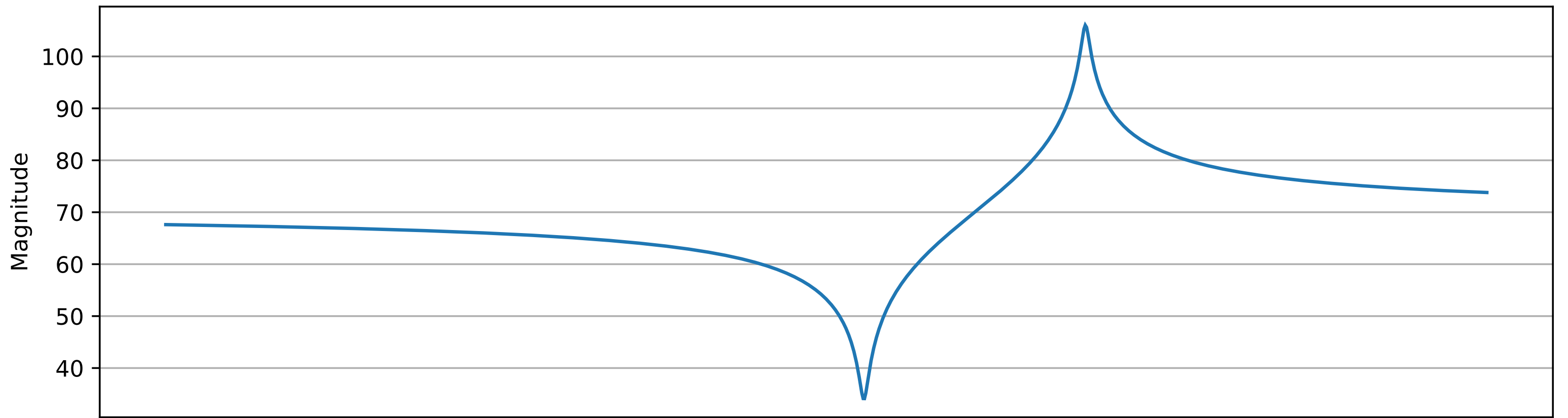
See [Crystal oscillator impedance](#) for a detailed explanation.



Negative transconductance compensate crystal series resistance


Long startup time caused by high Q

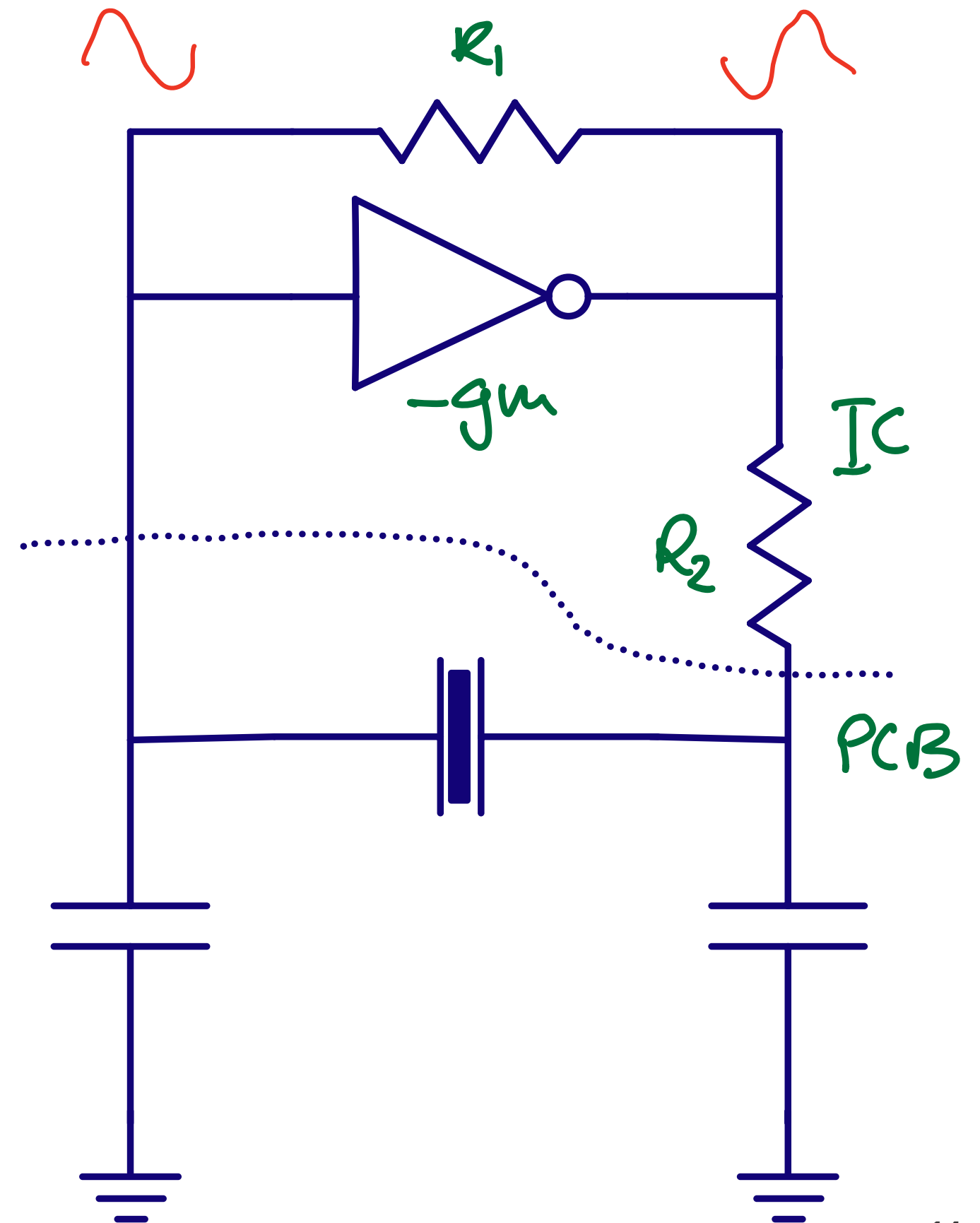Can fine tune frequency with parasitic capacitance




# Temperature Behaviour for AT Cut Crystals

$df / f$  [ ppm ]

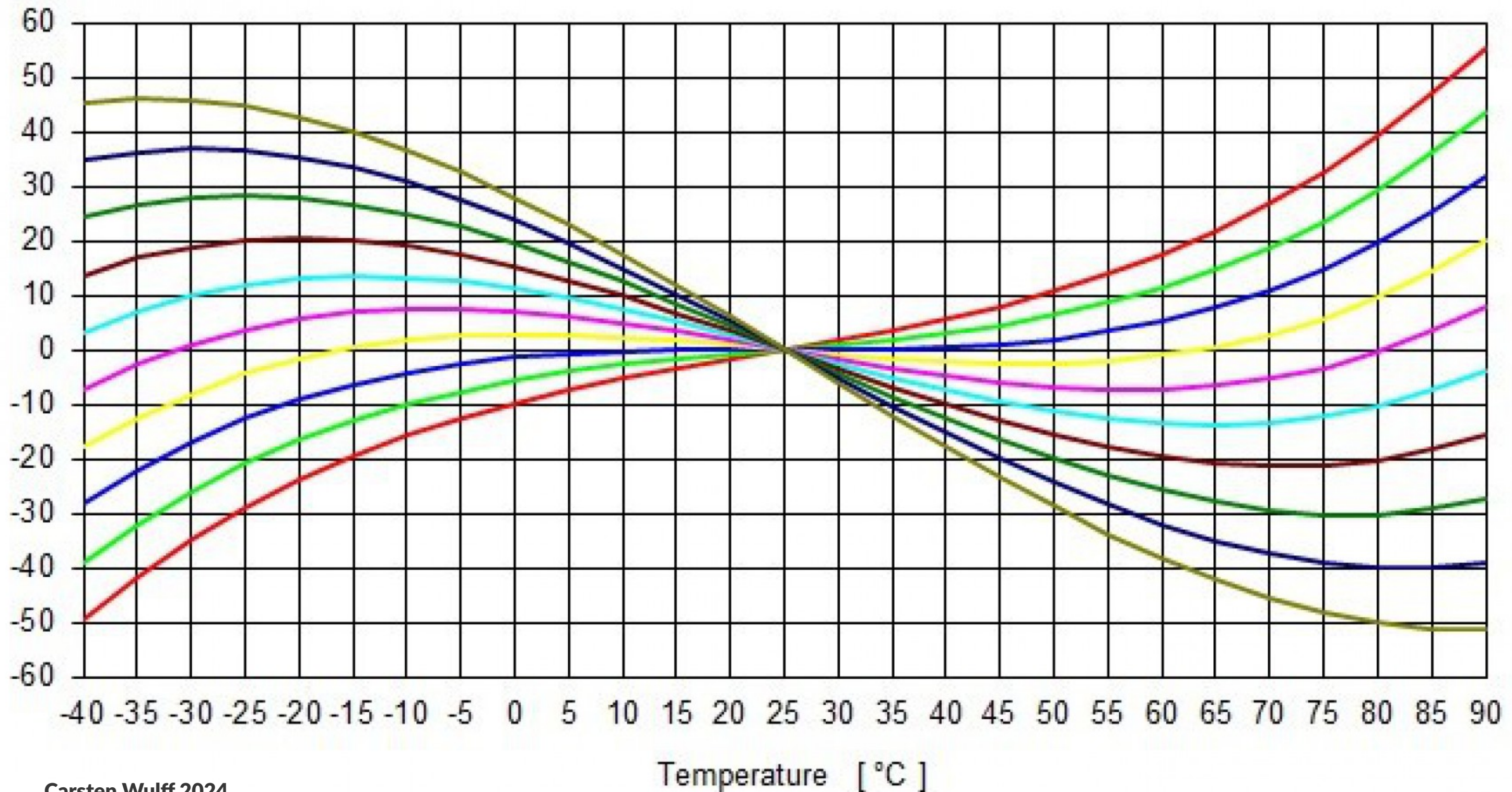


Cutting Angle [min]

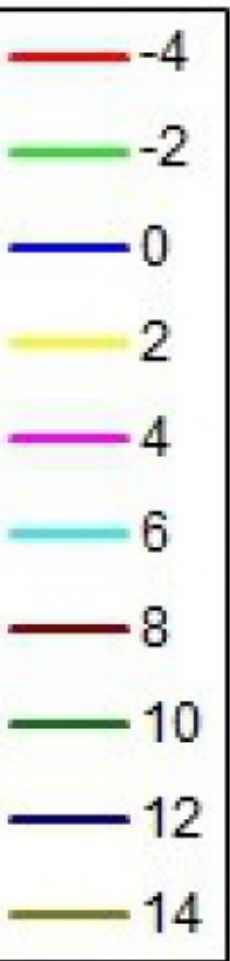

# Controlled Oscillators



# Ring oscillator

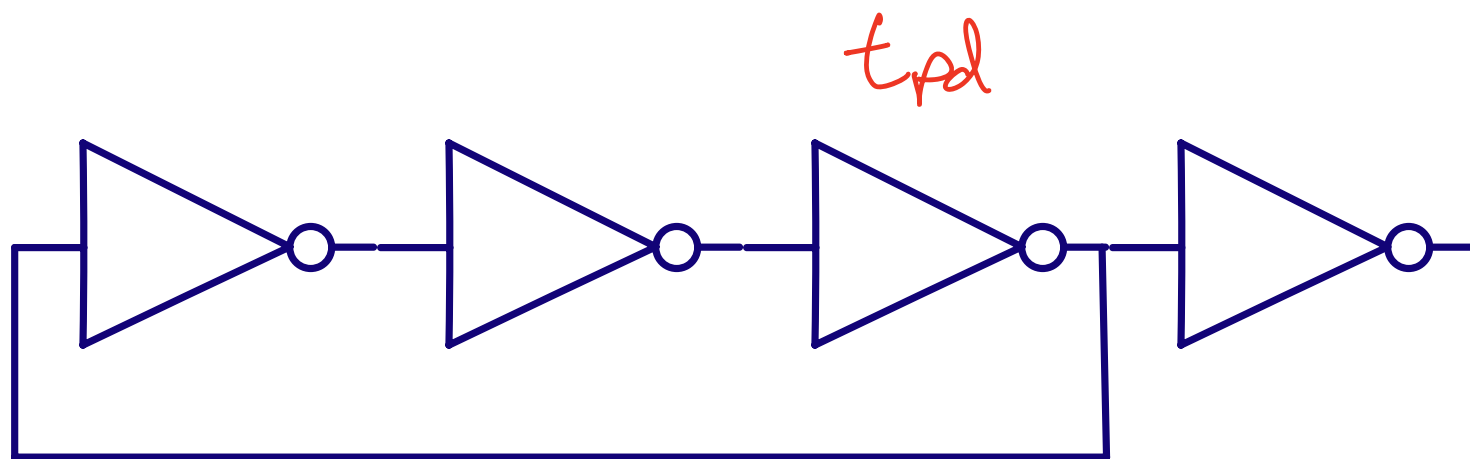

$$t_{pd} \approx RC$$

$$R \approx \frac{1}{gm} \approx \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{th})}$$


$$C \approx \frac{2}{3} C_{ox} WL$$

$$t_{pd} \approx \frac{2/3 C_{ox} W L}{\frac{W}{L} \mu_n C_{ox} (V_{DD} - V_{th})}$$

$$f = \frac{1}{2N t_{pd}} = \frac{\mu_n (V_{DD} - V_{th})}{\frac{4}{3} N L^2}$$

$$K_{vco} = 2\pi \frac{\partial f}{\partial V_{DD}} = \frac{2\pi \mu_n}{\frac{4}{3} N L^2}$$


# Capacitive load

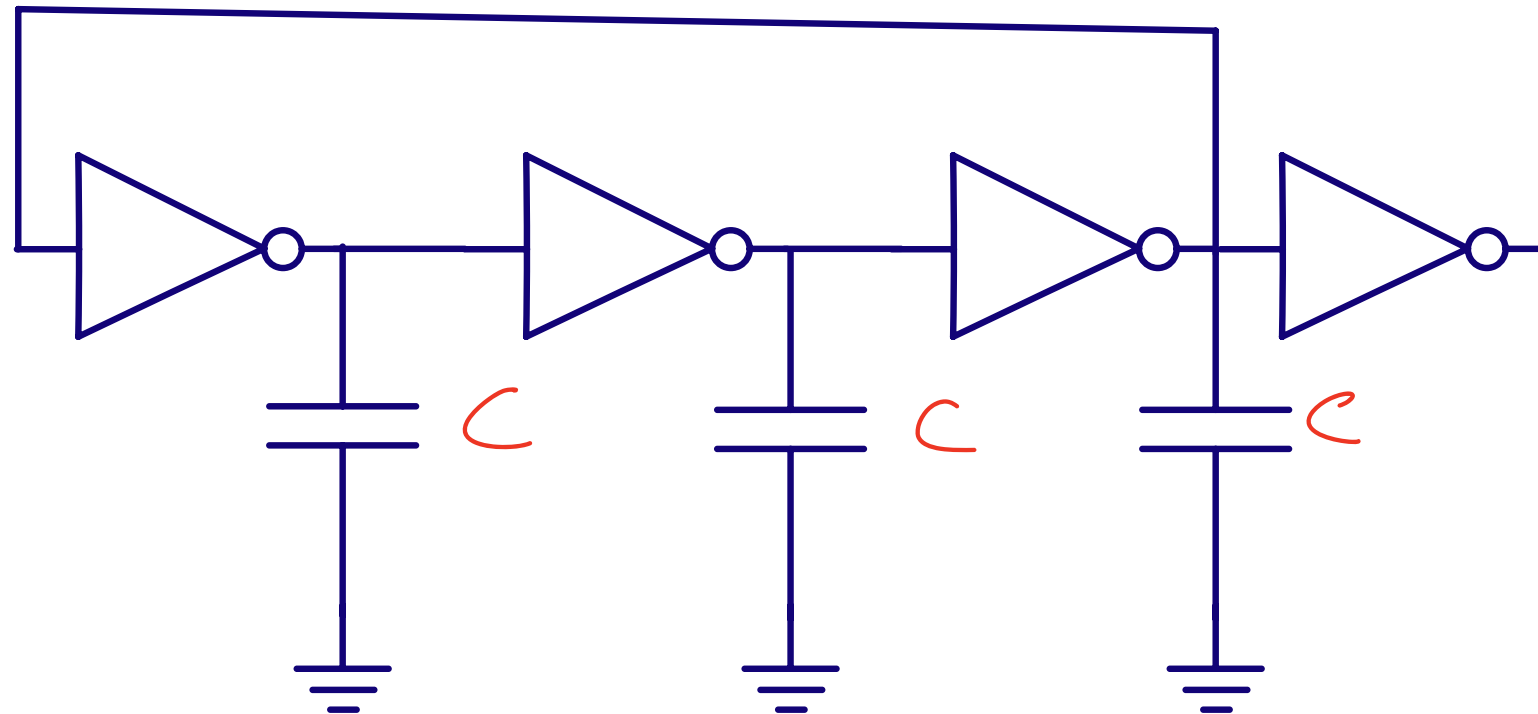

$$f = \frac{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{th})}{2N \left( \frac{2}{3} C_{ox} WL + C \right)}$$

$$K_{vco} = \frac{2\pi \mu_n C_{ox} \frac{W}{L}}{2N \left( \frac{2}{3} C_{ox} WL + C \right)}$$

# Realistic

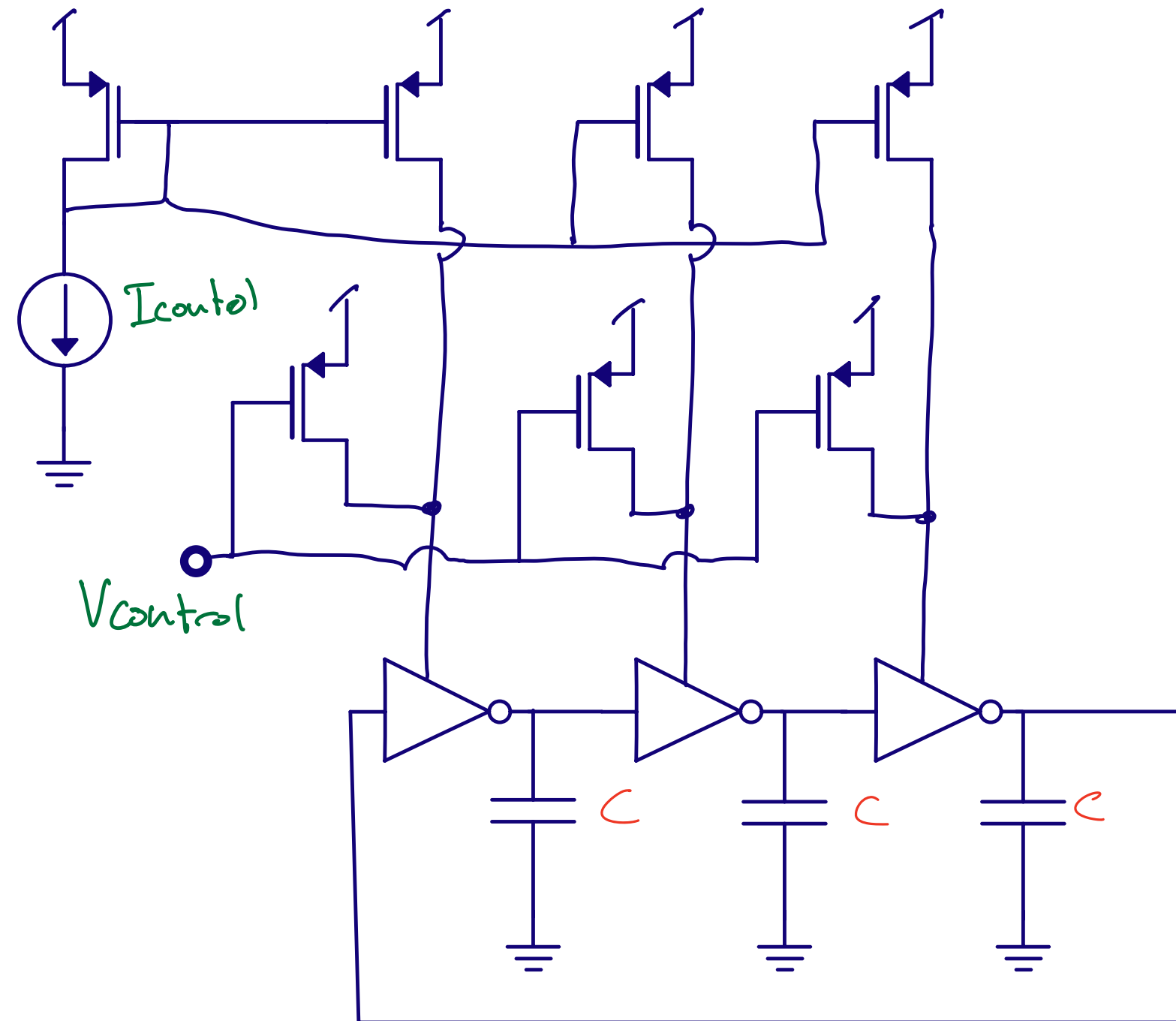


$$I = C \frac{dV}{dt}$$

$$f \approx \frac{I_{control} + \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{DD} - V_{control} - V_{th})^2}{C \frac{V_{DD}}{2} N}$$

$$K_{vco} = 2\pi \frac{\partial f}{\partial V_{control}}$$

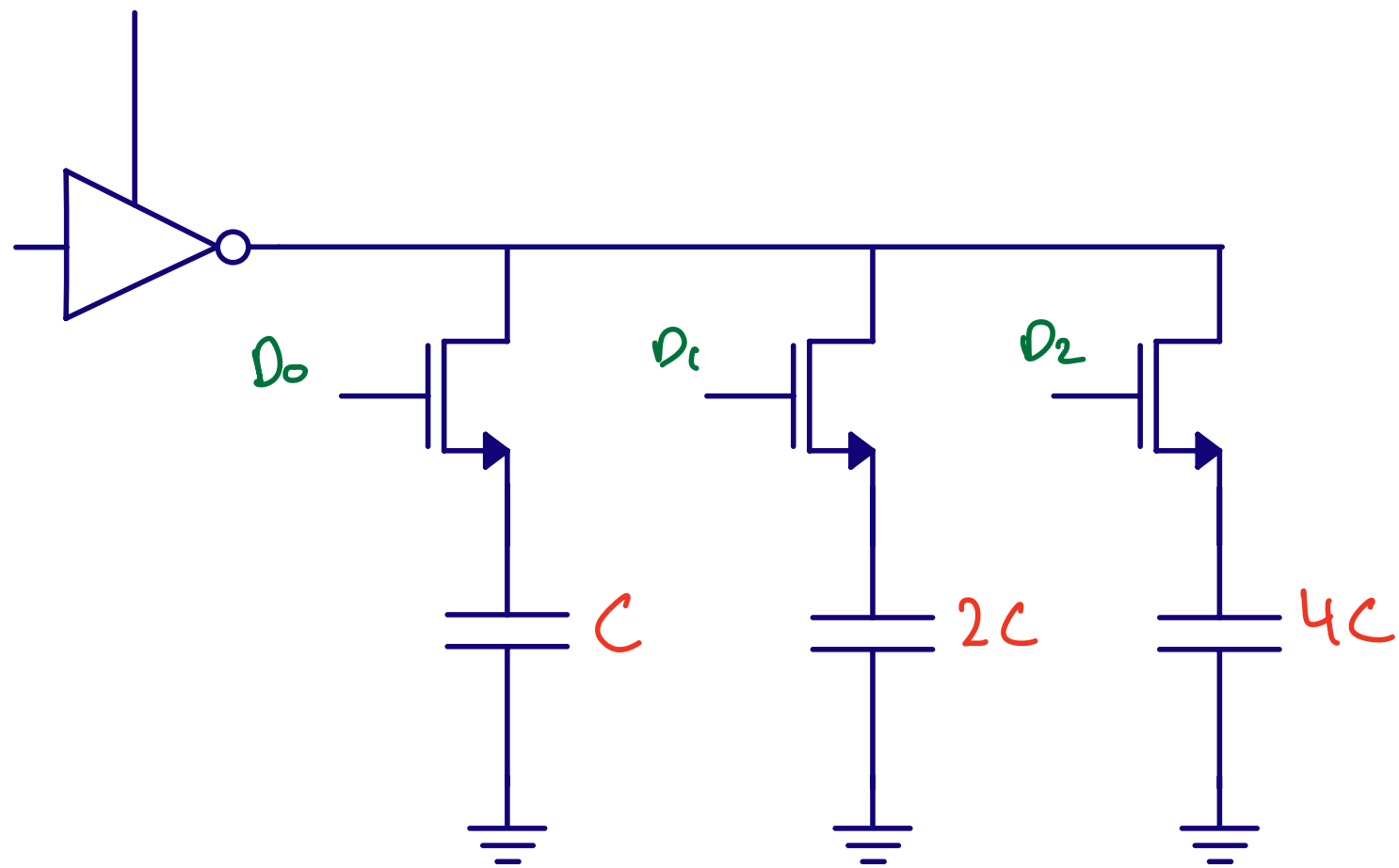
$$K_{vco} = 2\pi \frac{\mu_p C_{ox} W/L}{C \frac{V_{DD}}{2} N}$$




# Digitally controlled oscillator



# LC oscillator

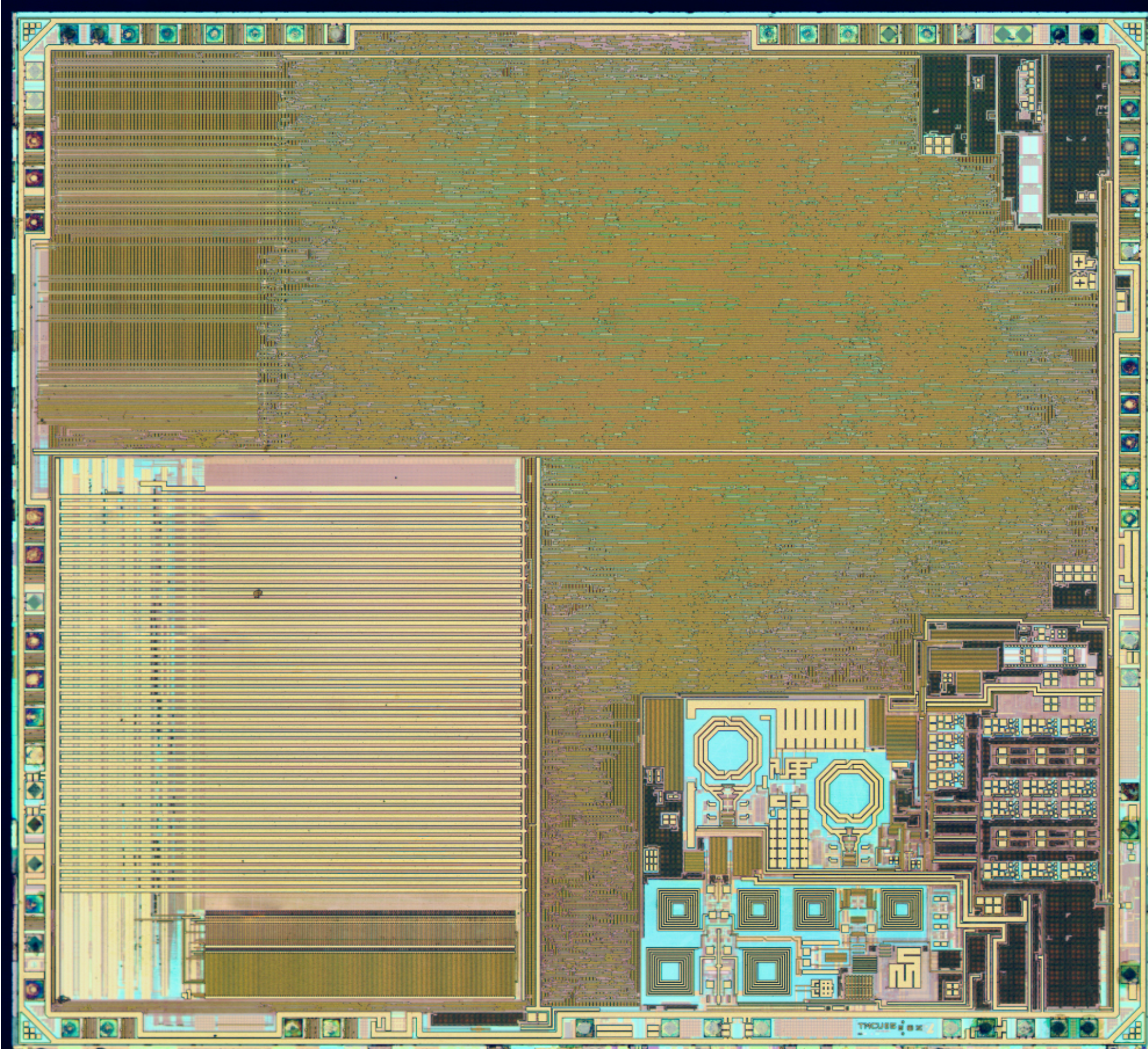





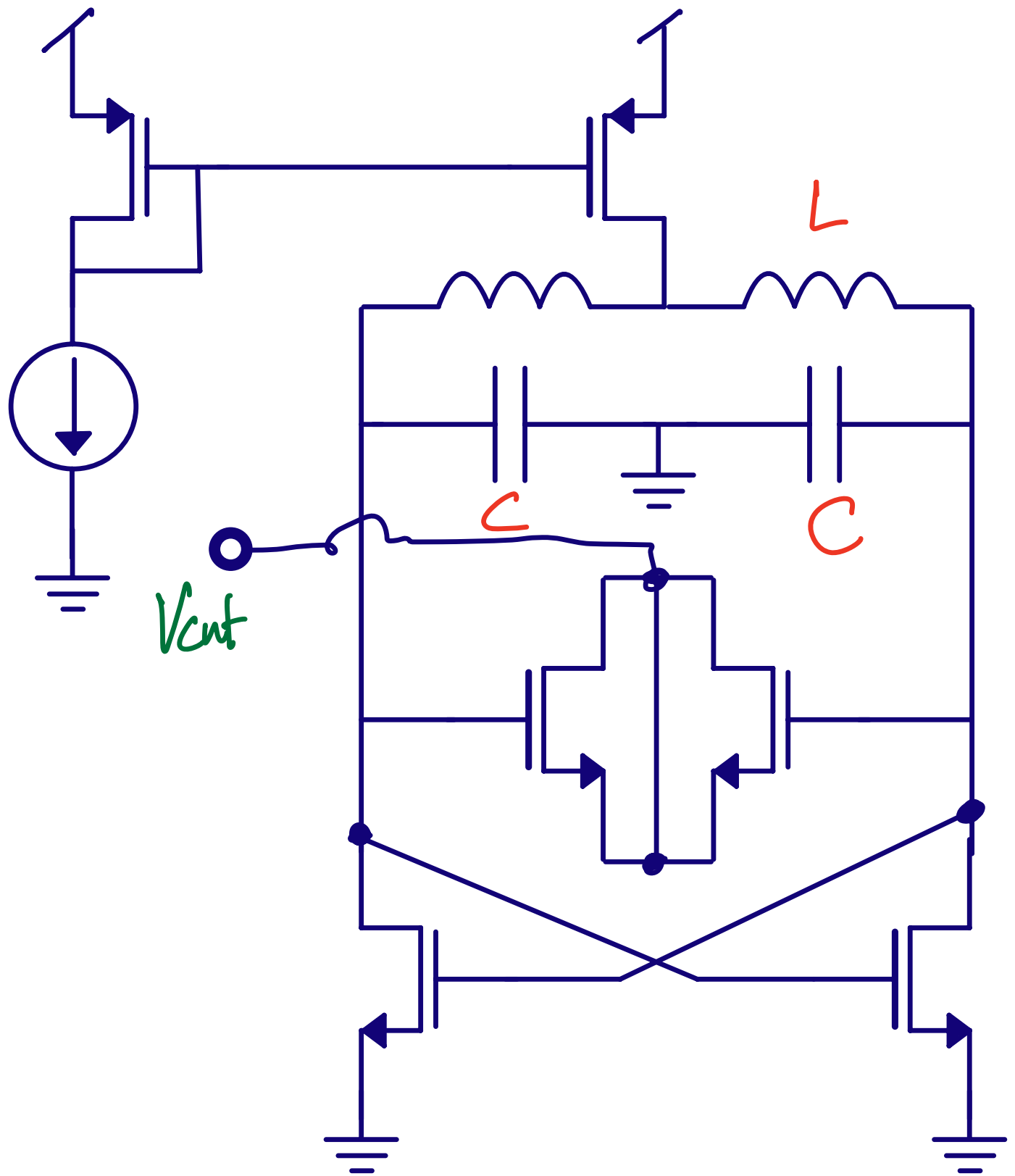

$$f \propto \frac{1}{\sqrt{LC}}$$

# Relaxation oscillators

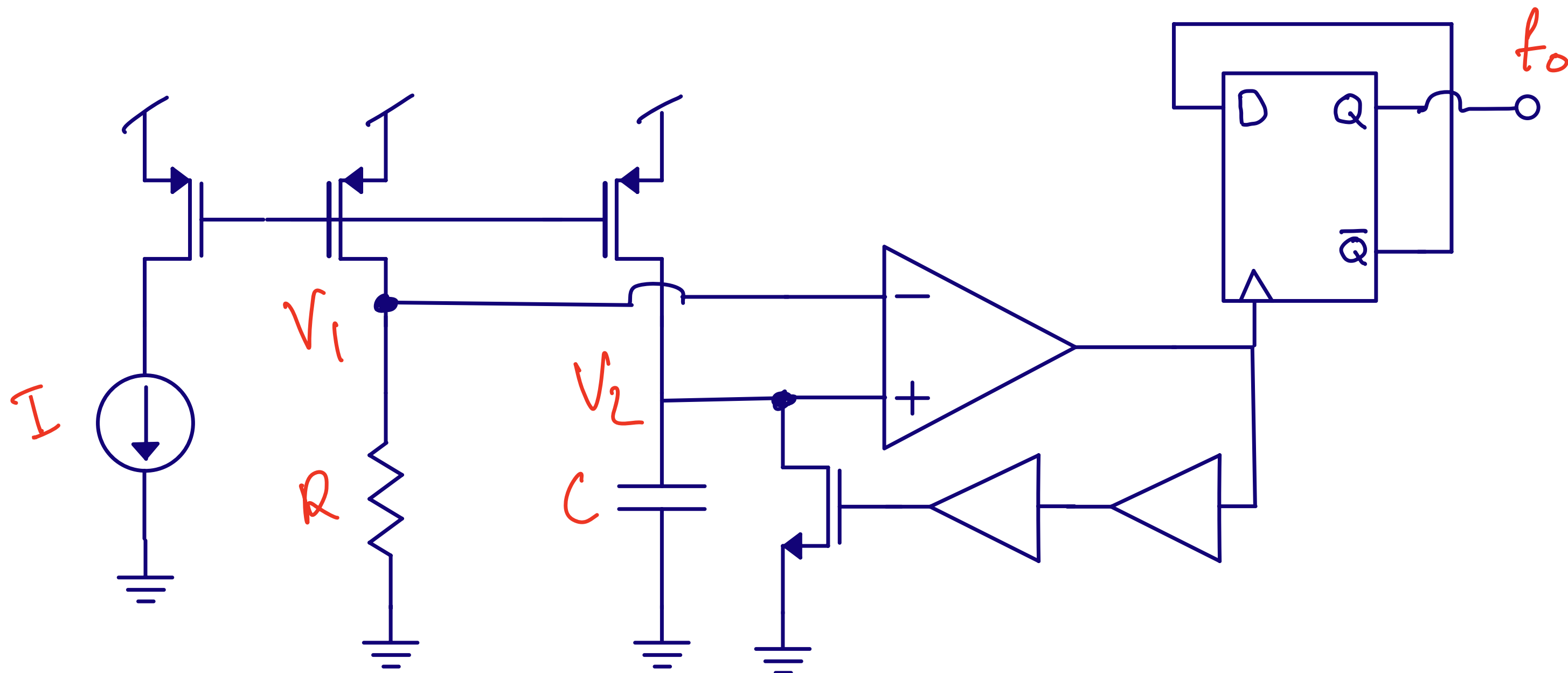

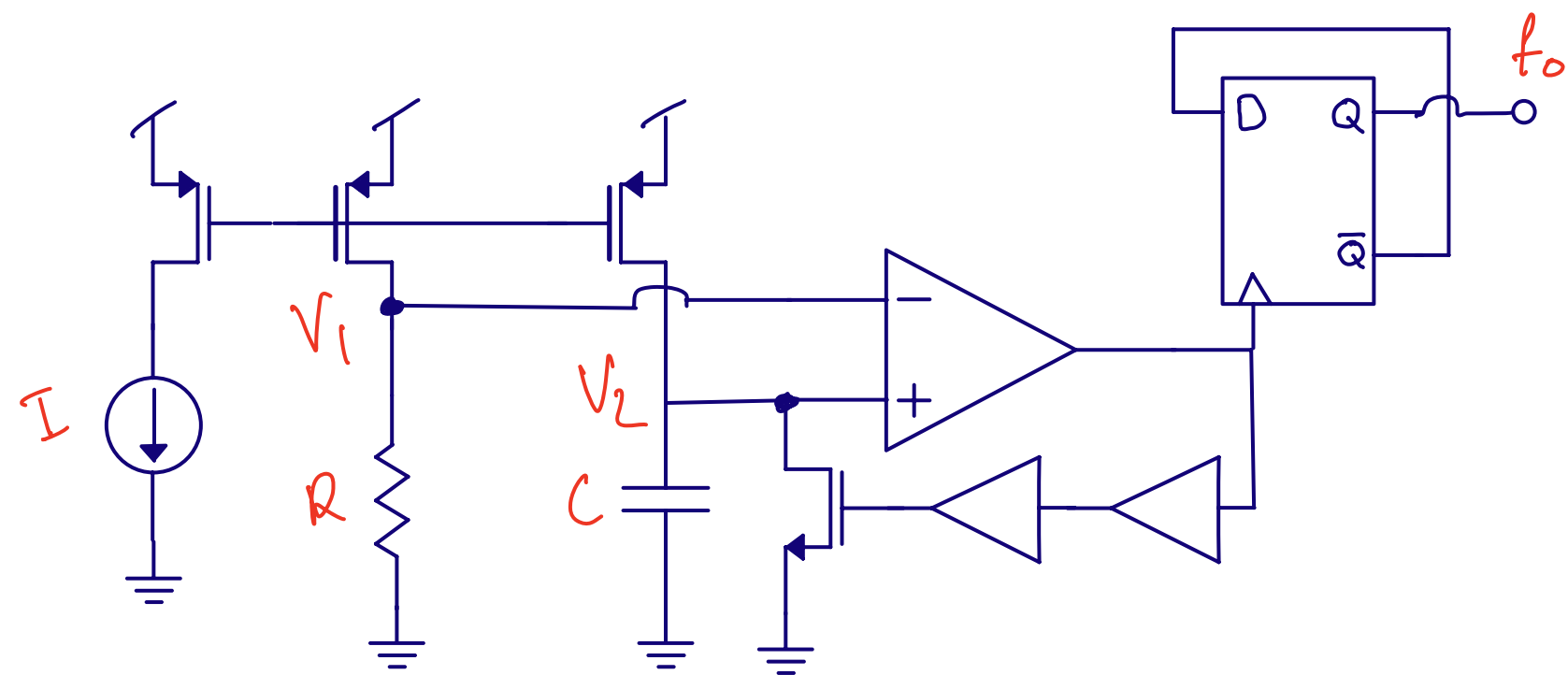

$$V_1 = IR$$

$$I = C \frac{dV}{dt}$$

$$dt = \frac{CV_2}{I} = \frac{CIR}{I}$$

$$f = \frac{1}{dt} = \frac{1}{RC}$$

$$f_o = \frac{1}{2} f = \frac{1}{2RC}$$

# Crystal oscillators

The Crystal Oscillator - A Circuit for All Seasons

High-performance crystal oscillator circuits: theory and application

Ultra-low Power 32kHz Crystal Oscillators: Fundamentals and Design Techniques

A Sub-nW Single-Supply 32-kHz Sub-Harmonic Pulse Injection Crystal Oscillator

# CMOS oscillators

The Ring Oscillator - A Circuit for All Seasons

A Study of Phase Noise in CMOS Oscillators

An Ultra-Low-Noise Swing-Boosted Differential Relaxation  
Oscillator in 0.18-um CMOS

Ultra Low Power Frequency Synthesizer

**Thanks!**