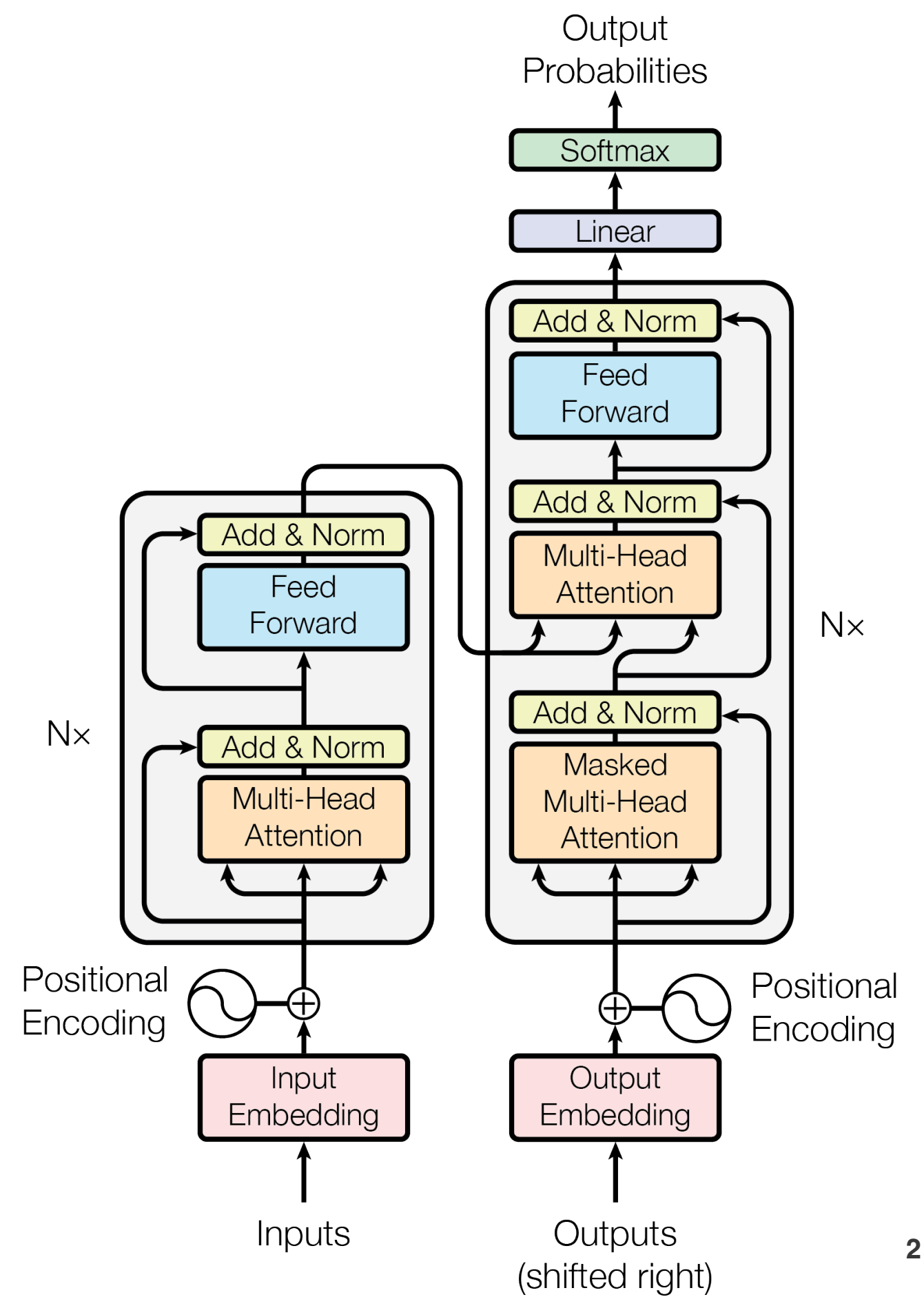


date: 2025-02-06


TFE4188

Analog Neural Networks

Attention Is All You Need




Neural Nets 3blue1brown

 

$$a_{l+1} = \sigma(W_l a_l + b_l)$$

 A NN consists of addition, multiplication,
and a non-linear function




$$\mathbf{y} = \sigma \left(\begin{bmatrix} w_{11} & w_{12} & \dots & w_{1n} \\ w_{21} & w_{22} & \dots & w_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ w_{m1} & w_{m2} & \dots & w_{mn} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix} + \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_m \end{bmatrix} \right)$$

$$\mathbf{OA}_{(x,y,k)} = f \left(\sum_{i=0}^{R-1} \sum_{j=0}^{S-1} \sum_{c=0}^{C-1} \mathbf{IA}_{(x+i,y+j,c)} \times \mathbf{W}_{(i,j,c,k)} \right)$$

Assume N neurons

- N multiplications per neuron
- N + 1 additions per neuron
- 1 sigmoid per neuron

 For efficient inference, additions and multiplications should be low power!




Adddition

Kirchhoff's circuit laws






Kirchoff's voltage law

The directed sum of the potential differences around any closed loop is zero

$$V_1 + V_2 + V_3 + V_4 = 0$$

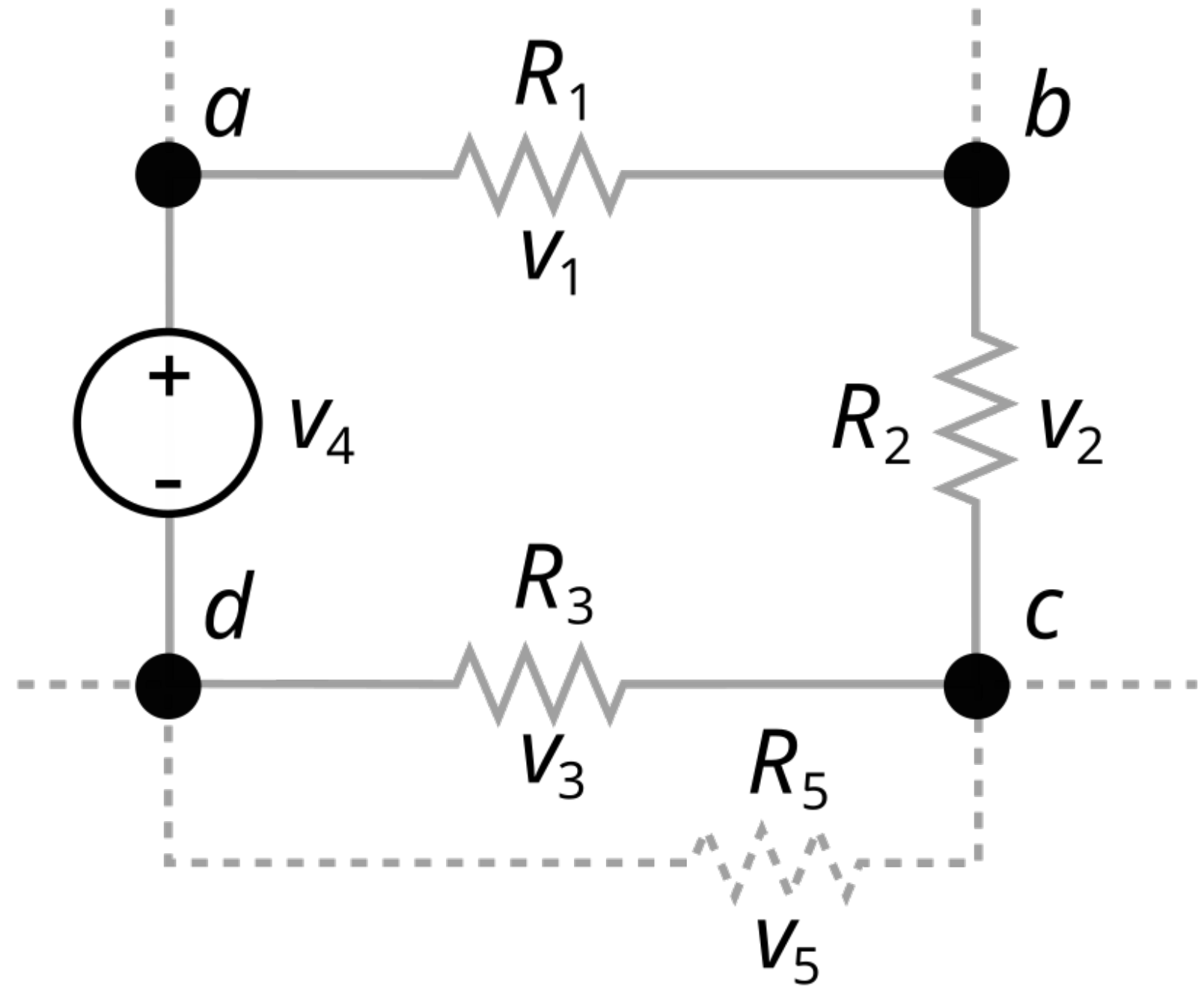


$$V_0 = V_1 + V_2 + V_3$$

     


Kirchoff's current law

The algebraic sum of currents in a network of conductors meeting at a point is zero

$$i_1 + i_2 + i_3 + i_4 = 0$$

 

 


Charge conservation

See [Charge conservation](#) on Wikipedia

$$Q_4 = Q_1 + Q_2 + Q_3$$
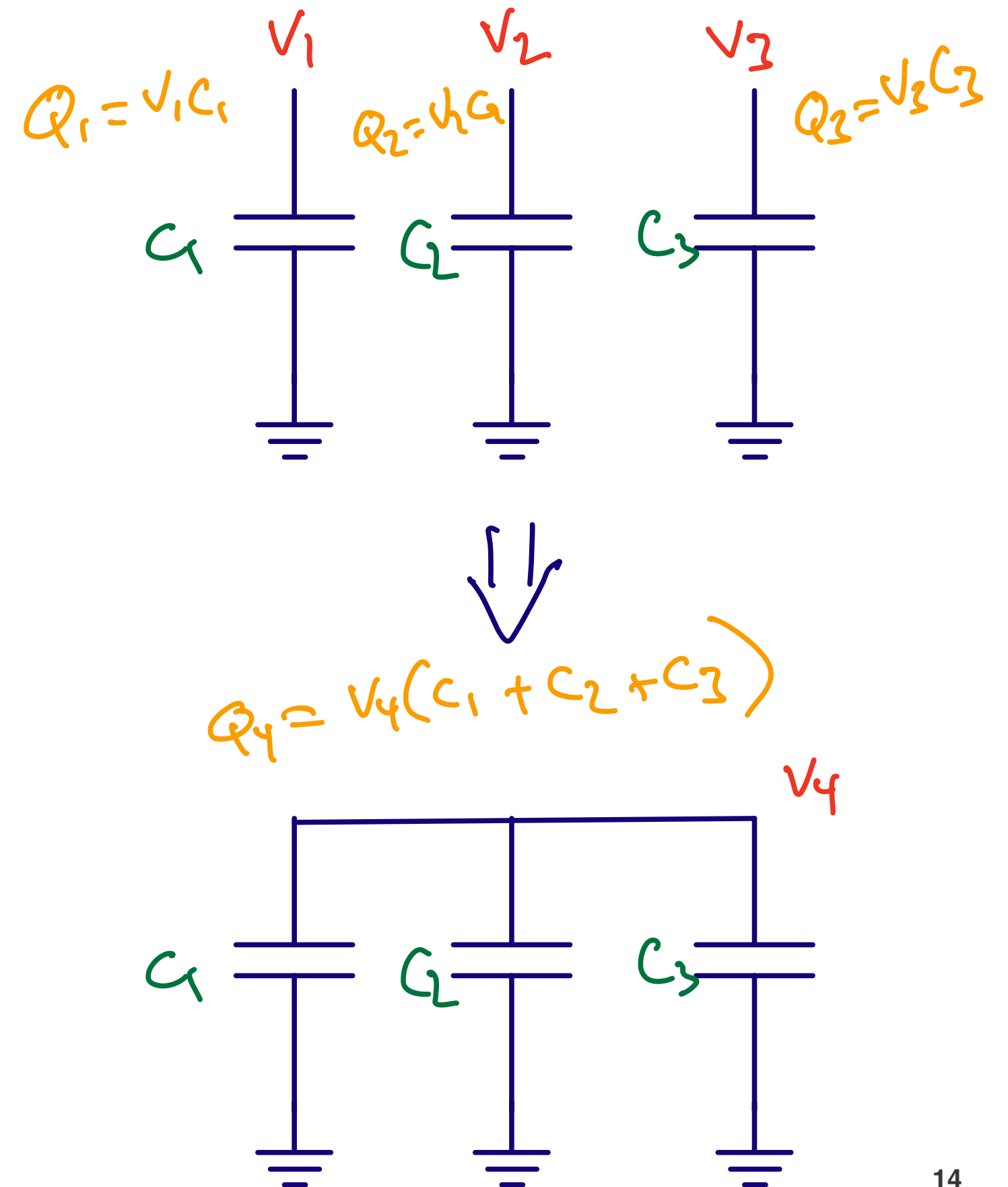
$$V_4 = \frac{C_1 V_1 + C_2 V_2 + C_3 V_3}{C_1 + C_2 + C_3}$$



Multiplication

Digital capacitance


$$V_4 = \frac{C_1 V_1 + C_2 V_2 + C_3 V_3}{C_1 + C_2 + C_3}$$

$$V_O = \frac{C_1}{C_{TOT}} V_1 + \dots + \frac{C_N}{C_{TOT}} V_N$$

Make capacitors digitally controlled, then

$$w_1 = \frac{C_1}{C_{TOT}}$$

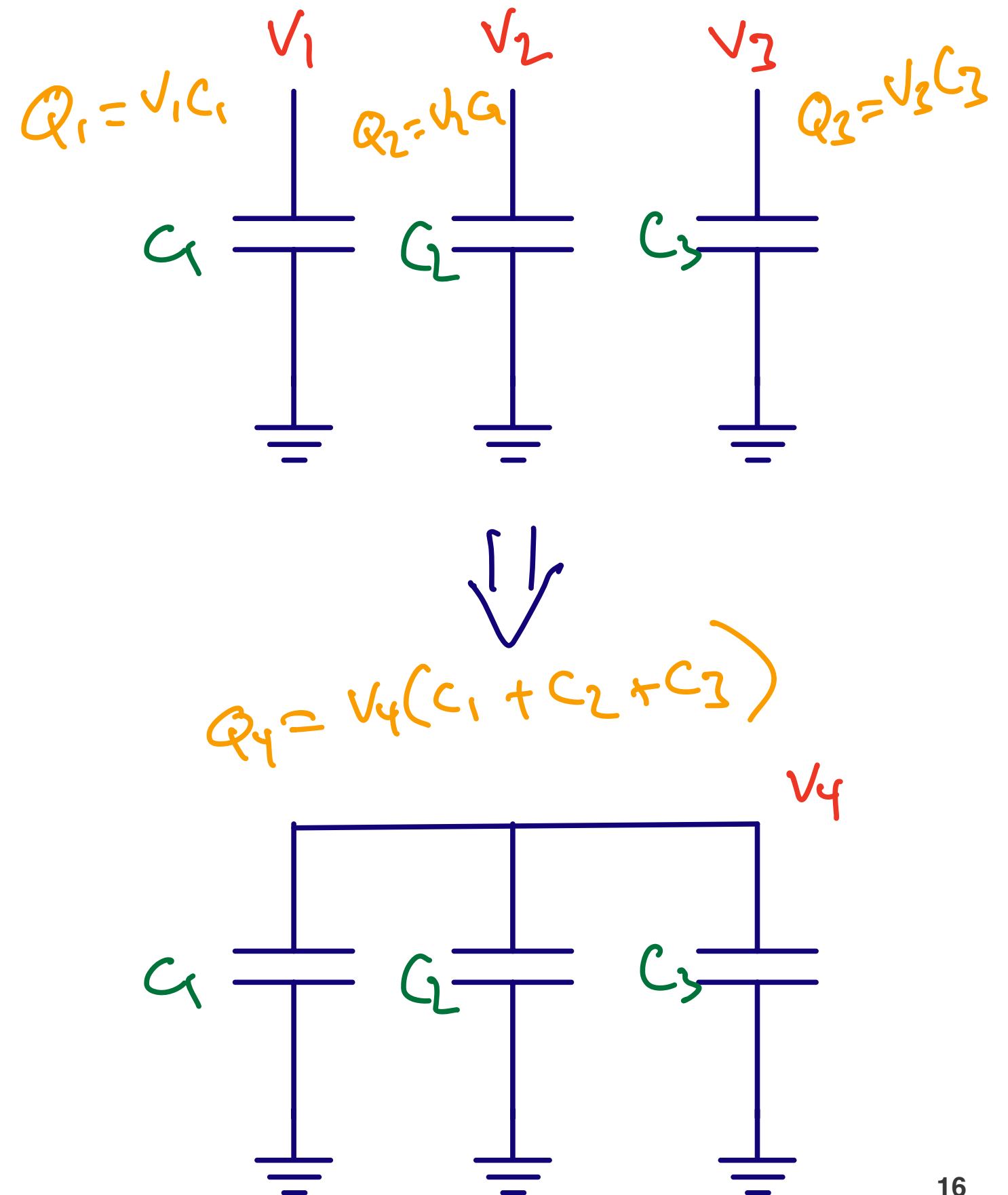
Might have a slight problem with variable gain as a function of total capacitance



Mixxing

$$I_{M1} = G_m V_{GS}$$

$$I_o = I_{M1} t_{input}$$

 


Translinear principle


MOSFET in sub-threshold

$$I = I_{D0} \frac{W}{L} e^{(V_{GS} - V_{th})/nU_T}, U_T = \frac{kT}{q}$$

$$I = \ell e^{V_{GS}/nU_T}, \ell = I_{D0} \frac{W}{L} e^{-V_{th}/nU_T}$$
 
$$V_{GS} = nU_T \ln\left(\frac{I}{\ell}\right)$$



 


$$V_1 + V_2 = V_3 + V_4$$

$$nU_T \left[\ln\left(\frac{I_1}{l_1}\right) + \ln\left(\frac{I_2}{l_2}\right) \right] = nU_T \left[\ln\left(\frac{I_3}{l_3}\right) + \ln\left(\frac{I_4}{l_4}\right) \right]$$

$$\ln\left(\frac{I_1 I_2}{l_1 l_2}\right) = \ln\left(\frac{I_3 I_4}{l_3 l_4}\right)$$

$$\frac{I_1 I_2}{l_1 l_2} = \frac{I_3 I_4}{l_3 l_4}$$
 
$$I_1 I_2 = I_3 I_4, \text{ if } l_1 l_2 = l_3 l_4$$



$$I_1 I_2 = I_3 I_4$$

$$I_1 = I_a, I_2 = I_b + i_b, I_3 = I_b, I_4 = I_a + i_a$$

$$I_a(I_b + i_b) = I_b(I_a + i_a)$$

$$I_a I_b + I_a i_b = I_b I_a + I_b i_a$$

$$i_b = \frac{I_b}{I_a} i_a$$

$$l_1 l_2 = l_3 l_4$$

$$l_1 = I_{D0} \frac{W}{L} e^{-V_{th}/nU_T}$$

$$l_2 = I_{D0} \frac{W}{L} e^{-(V_{th} \pm \sigma_{th})/nU_T} = l_1 e^{\pm \sigma_{th}/nU_T}$$

$$\sigma_{th} = \frac{a_{vt}}{\sqrt{WL}}$$

$$\frac{l_2}{l_1} = e^{\pm \frac{a_{vt}}{\sqrt{WL}}/nU_T}$$

Demo

JNW_SV_SKY130A

Want to learn more?

An Always-On 3.8 μ J/86 % CIFAR-10 Mixed-Signal Binary CNN Processor With All Memory on Chip in 28-nm CMOS

CAP-RAM: A Charge-Domain In-Memory Computing 6T-SRAM for Accurate and Precision-Programmable CNN Inference

ARCHON: A 332.7TOPS/W 5b Variation-Tolerant Analog CNN Processor Featuring Analog Neuronal Computation Unit and Analog Memory

IMPACT: A 1-to-4b 813-TOPS/W 22-nm FD-SOI Compute-in-Memory CNN Accelerator Featuring a 4.2-POPS/W 146-TOPS/mm² CIM-SRAM With Multi-Bit Analog Batch-Normalization

Thanks!